



Please write clearly in block capitals.

Centre number

--	--	--	--	--

Candidate number

--	--	--	--

Surname

---

Forename(s)

---

Candidate signature

---

# Level 3 Certificate and Extended Certificate in Applied Science KEY CONCEPTS IN SCIENCE

Unit Number: ASC1

Section C – ASC1/P (Physics)

Tuesday 23 January 2018

Morning

Time allowed: 1 hour 30 minutes

You are advised to spend  
approximately 30 minutes on  
this section.

## Materials

For this paper you must have:

- a calculator
- formulae sheet.

## Instructions

- Use black ink or black ball-point pen.
- Answer **all** questions in each section.
- You must answer the questions in the spaces provided.
- Do not write outside the box around each page or on blank pages.
- Do all rough work in this book. Cross through any work you do not want to be marked.

## Information

- You will be provided with a copy of the formulae sheet.
- There are three sections in this paper:  
**Section A** – Biology **Section B** – Chemistry **Section C** – Physics.
- The marks for questions are shown in brackets.
- The maximum mark for this paper is 60 and the maximum mark for this section is 20.

## Advice

Read each question carefully.

For Examiner's Use	
Examiner's Initials	
Question	Mark
1	
2	
TOTAL	



J A N 1 8 A S C 1 P O 1

G/TI/Jan18/E5

**ASC1/P**

**Section C – Physics**Answer **all** questions in this section.

0 1

Power stations which use renewable energy resources produce around 25% of the United Kingdom's electricity.

0 1 . 1

**Table 1** shows different types of power station.

Tick (✓) **all** of the power stations in **Table 1** which use renewable energy sources.  
[1 mark]

**Table 1**


Type of power station	Tick (✓)
Biomass	
Coal	
Geothermal	
Natural gas	
Nuclear	
Oil	
Wave	
Wind	

Hydroelectric power is another type of renewable energy.

**Figure 1** shows a hydroelectric power station.

The hydroelectric power station has a power output of 440 MW when water passes through it.

Water is supplied from a reservoir.

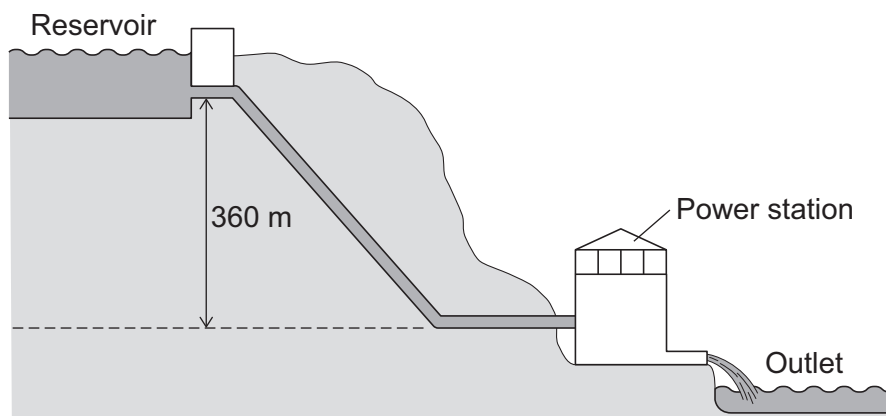**Figure 1**

0 1 . 2

167 000 kg of water flow through the power station each second.

Calculate the loss of gravitational potential energy per second of the water as it flows from the reservoir to the power station.

Give an appropriate unit for your answer.

Assume  $g = 9.8 \text{ ms}^{-2}$

[3 marks]

Loss of gravitational potential energy per second = \_\_\_\_\_ Unit = \_\_\_\_\_

0 1 . 3

Calculate the efficiency of the hydroelectric power station.

[2 marks]

Efficiency = \_\_\_\_\_

0 1 . 4

State **two** ways in which energy could be wasted in the hydroelectric power station.

[2 marks]

1 \_\_\_\_\_

\_\_\_\_\_

2 \_\_\_\_\_

\_\_\_\_\_

Question 1 continues on the next page

Turn over ►



Do not write  
outside the  
box

0 1 . 5

Nuclear power stations produce approximately 20% of the United Kingdom's electricity.

Describe how electricity is generated in a nuclear power station.

[4 marks]

---

---

---

---

---

---

---

---

---

---

0 1 . 6

State **one** disadvantage to the environment of using a nuclear power station to generate electricity.

[1 mark]

---

---

13




0 2

A technician has set up four electrical circuits. She uses three identical  $10\ \Omega$  resistors in each circuit.

**Figure 2** shows the arrangement of resistors in each circuit.

**Figure 2**

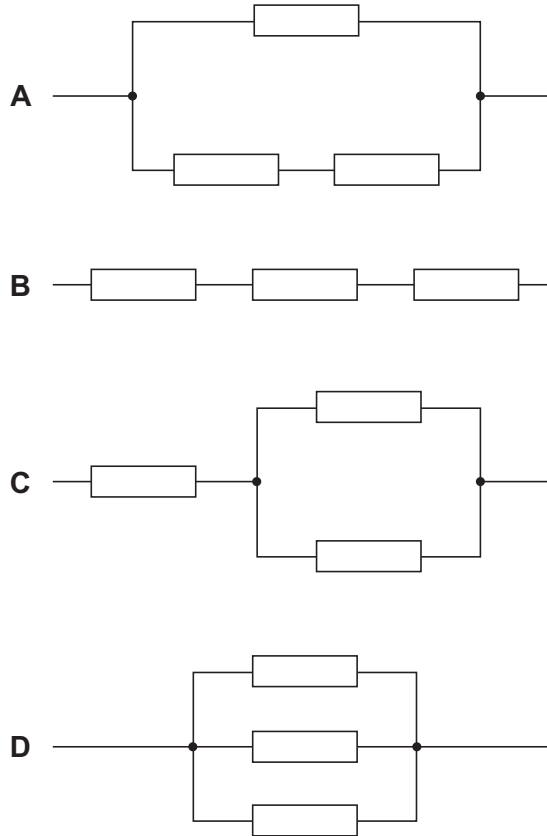

0 2 . 1

State which circuit, **A**, **B**, **C** or **D**, has the **lowest** total resistance and which has the **highest** total resistance.

[2 marks]

Lowest total resistance \_\_\_\_\_

Highest total resistance \_\_\_\_\_


**Question 2 continues on the next page**

Turn over ►



The technician uses **two** of the identical  $10\ \Omega$  resistors in a circuit as shown in **Figure 3**.

**Figure 3**

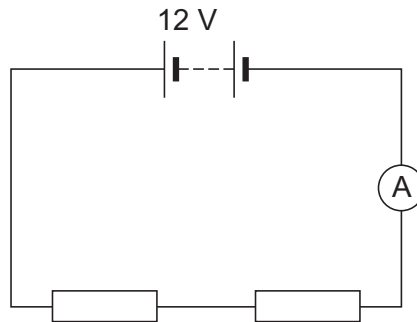

- 0 2 . 2** Add a component to **Figure 3** which would allow the technician to measure the voltage across **one** of the resistors.

[1 mark]

- 0 2 . 3** Calculate the reading on the ammeter in **Figure 3**.

[2 marks]

Reading on ammeter = \_\_\_\_\_ A

- 0 2 . 4** State what the expected voltage across each resistor should be.

[1 mark]

Voltage = \_\_\_\_\_ V



0 2 . 5

The technician measures the voltage across **one** of the resistors. The voltage is less than she expects it to be.

Give **one** reason why the voltage is lower than expected.

[1 mark]

---

---

7

**END OF QUESTIONS**



**There are no questions printed on this page**

*Do not write  
outside the  
box*

**DO NOT WRITE ON THIS PAGE  
ANSWER IN THE SPACES PROVIDED**

**Copyright information**

For confidentiality purposes, from the November 2015 examination series, acknowledgements of third party copyright material will be published in a separate booklet rather than including them on the examination paper or support materials. This booklet is published after each examination series and is available for free download from [www.aqa.org.uk](http://www.aqa.org.uk) after the live examination series.

Permission to reproduce all copyright material has been applied for. In some cases, efforts to contact copyright-holders may have been unsuccessful and AQA will be happy to rectify any omissions of acknowledgements. If you have any queries please contact the Copyright Team, AQA, Stag Hill House, Guildford, GU2 7XJ.

Copyright © 2018 AQA and its licensors. All rights reserved.

