

Q1

5 (a)	(i)	resistance = V/I C1	
		= $6.0/(40 \times 10^{-3})$ = 150Ω A1	
		(no marks for use of gradient)	
	(ii)	at 8.0 V, resistance = $8.0/(50 \times 10^{-3}) = 160 \Omega$ C1	
		change = 10Ω A1	[4]
(b)	(i)	straight line through origin M1	
		passes through $I = 40 \text{ mA}$, $V = 8.0\text{V}$ A1	
	(ii)	current in both must be 40 mA C1	
		e.m.f. = $8.0 + 6.0 = 14.0 \text{ V}$ A1	[4]

Q2.

7 (a)	(i)	$P = VI$ C1	
		current = $60/240 = 0.25 \text{ A}$ A1	
	(ii)	$R (= V/I) = 240/0.25$ M1	
		= 960Ω A0	[3]
(b)		$R = \rho L/A$ (wrong formula, 0/3) C1	
		$960 = (7.9 \times 10^{-7} \times L)/(\pi \times (6.0 \times 10^{-6})^2)$ C1	
		$L = 0.137 \text{ m}$ A1	[3]
		(use of $A = 2\pi r$, then allow 1/3 marks only for resistivity formula)	
(c)		e.g. the filament must be coiled/it is long for a lamp B1	[1]
		(allow any sensible comment based on candidate's answer for L)	
Total			[7]

Q3.

8 (a)		$V/E = R/R_{\text{tot}}$ C1	
		$1.0/1.5 = R/(R + 3900)$ M1	
		$R = 7800\Omega$ A0	[2]
(b)		$V = 1.5 \times (7800/(7800 + 1250))$ C1	
		= 1.29 V A1	[2]
		or $I = 1.5/(7800 + 1250)$ or $V = IR = 1.29 \text{ V}$	
(c)		Combined resistance of R and voltmeter is 3900Ω C1	
		reading at 0°C is 0.75 V A1	[2]
Total			[6]

Q4.

6	(a) (i)	lines normal to plate and equal spacing (at least 4 lines) direction from (+) to earthed plate	B1 B1	[2]
	(ii)	$E = 160/0.08$ $= 2.0 \times 10^3 \text{ V m}^{-1}$	M1 A0	[1]
	(b) (i)	correct directions with line of action of arrows passing through charges	B1	[1]
	(ii)	force $= Eq$ $= 2.0 \times 10^3 \times 1.2 \times 10^{-15}$ $= 2.4 \times 10^{-12} \text{ N}$	C1 A1	[2]
	(iii)	couple = force \times perpendicular separation $= 2.4 \times 10^{-12} \times 2.5 \times 10^{-3} \times \sin 35^\circ$ $= 3.4(4) \times 10^{-15} \text{ N m}$	M1 A1	[2]
	(iv)	either rotates to align with the field or oscillates (about a position) with the positive charge nearer to the earthed plate/clockwise	M1 A1	[2]
Q5.				
7	(a)	potential difference/current	B1	[1]
	(b) (i)	1) 1.13 W 2) 1.50 V	B1	[1]
	(ii)	power $= V^2 / R$ or power $= VI$ and $V = IR$ $R = 1.50^2 / 1.13$ $= 1.99 \Omega$	C1 A1	[2]
	(iii)	either $E = IR + Ir$ or voltage divided between R and r $I = 1.5 / 2.0 (=0.75 \text{ A})$ p.d. across $R =$ p.d. across $r = 1.5$ $3.0 = 1.5 + 0.75r$ $r = 2.0 \Omega$ so $R = r = 1.99 \Omega$	C1 C1 A1	[3]
	(c)	larger p.d. across R means smaller p.d. across r smaller power dissipation at larger value of V since power is VI and I is same for R and r	M1 A1 A1	[3]
Q6.				

7	(a) lamp C lamp is shorted	M1 A1	[2]
	(b) shorted lamp A would cause damage to the supply/lamps /blow fuse in supply	B1	[1]
	(c) 15 Ω	B1	[1]
	(d) (i) $V = IR$ $R = 30 \Omega$	C1 A1	[2]
	(ii) $P = VI$ or I^2R or V^2/R $P = 1.2 \text{ W}$	C1 A1	[2]
	(e) filament is cold when measuring with ohm-meter in (b) resistance of filament rises as temperature rises	B1 B1	[2]

Q7.

2	(a) force per unit positive charge (on a small test charge)	B1	[1]
	(b) field strength = $(210 / \{1.5 \times 10^{-2}\}) = 1.4 \times 10^4 \text{ N C}^{-1}$	A1	[1]
	(c) (i) acceleration = Eq / m $= (1.4 \times 10^4 \times 1.6 \times 10^{-19}) / (9.1 \times 10^{-31})$ $= 2.5 \times 10^{15} \text{ m s}^{-2}$ (2.46 × 10 ¹⁵) towards positive plate / upwards (and normal to plate)	C1 C1 A1 B1	[4]
	(ii) time = $2.4 \times 10^{-9} \text{ s}$	A1	[1]
	(d) either vertical displacement after acceleration for $2.4 \times 10^{-9} \text{ s}$ $= \frac{1}{2} \times 2.46 \times 10^{15} \times (2.4 \times 10^{-9})^2$ $= 7.1 \times 10^{-3} \text{ m}$ (0.71 cm < 0.75 cm and) so will pass between plates <i>i.e. valid conclusion based on a numerical value</i>	C1 A1 A1	[3]
	or $0.75 \times 10^{-2} = \frac{1}{2} \times 2.46 \times 10^{15} \times t^2$ t is time to travel 'half-way across' plates = $2.47 \times 10^{-9} \text{ s}$ (2.4 ns < 2.47 ns) so will pass between plates <i>i.e. valid conclusion based on a numerical value</i>	(C1) (A1) (A1)	

Q8.

- 6 (a) (i) 1 total resistance = 0.16Ω A1
 2 e.m.f. = either $(14 - E)$ or $(E - 14)$ A1 [2]
- (ii) either $14 - E = 42 \times 0.16$ or $(E - 14) = -42 \times 0.16$ C1
 $E = 7.3 \text{ V}$ A1 [2]
- (b) (i) charge = It C1
 $= 12.5 \times 4 \times 60 \times 60$
 $= 1.8 \times 10^5 \text{ C}$ A1 [2]
- (ii) either energy = EQ or energy = Et C1
 either energy = $14 \times 1.8 \times 10^5$ or energy = $14 \times 12.5 \times 4 \times 3600$
 $= 2.52 \times 10^6 \text{ J}$ A1 [2]
- (iii) energy = I^2Rt or Vit and $V = IR$ C1
 $= 12.5^2 \times 0.16 \times 4 \times 3600$
 $= 3.6 \times 10^5 \text{ J}$ A1 [2]
- (c) efficiency = $(2.52 \times 10^6 - 3.6 \times 10^5) / (2.52 \times 10^6)$ C1
 $= 86\%$ A1 [2]

Q9.

- 6 (a) either $P = VI$ and $V = IR$ or $P = V^2 / R$ C1
 resistance = 38.4Ω A1 [2]
- (b) zero B1
 1.5 kW B1
 3.0 kW B1
 0.75 kW B1
 2.25 kW B1 [5]

Q10.



- 6 (a) (i) $E = V/d$ C1
 $= 350 / (2.5 \times 10^{-2})$
 $= 1.4 \times 10^4 \text{ N C}^{-1}$ A1 [2]
- (ii) force = Eq C1
 $= 1.4 \times 10^4 \times 1.6 \times 10^{-19}$ M1
 $= 2.24 \times 10^{-15}$ A0 [2]
- (b) (i) $F = ma$ C1
 $a = (2.24 \times 10^{-15}) / (9.1 \times 10^{-31})$
 $= 2.46 \times 10^{15} \text{ m s}^{-2}$... (allow 2.5×10^5) A1 [2]
- (ii) $s = \frac{1}{2}at^2$ C1
 $2.5 \times 10^{-2} = \frac{1}{2} \times 2.46 \times 10^{15} \times t^2$
 $t = 4.5 \times 10^{-9} \text{ s}$ A1 [2]
- (c) either gravitational force is normal to electric force
or electric force horizontal, gravitational force vertical B2 [2]
special case: force/acceleration due to electric field \gg force/acceleration
due to gravitational field, allow 1 mark

Q11.

- 7 (a) (i) R B1 [1]
(ii) $0.5R$ B1 [1]
(iii) $2.5R$... (allow e.c.f. from (ii)) B1 [1]
- (b) (i) $I_1 + I_2 = I_3$ B1 [1]
(ii) $E_2 = I_3R + I_2R$ B1 [1]
(iii) $E_1 - E_2 = 2I_1R - I_2R$ B1 [1]

Q12.

- 7 (a) ∞ A1
 $2R$ A1
 R A1 [3]
- (b) (i) $I_1 + I_3 = I_2 + I_4$ A1 [1]
(ii) $E_2 - E_1 = I_3R$ A1 [1]
(iii) $E_2 = I_3R + 2I_4R$ A1 [1]

Q13.

- 5 (a) region/area where a charge experiences a force B1 [1]
- (b) (i) left-hand sphere (+), right-hand sphere (-) B1 [1]
- (ii) 1 correct region labelled C within 10 mm of central part of plate
otherwise within 5 mm of plate B1 [1]
- 2 correct region labelled D area of field not included for (b)(ii)1 B1 [1]
- (c) (i) arrows through P and N in correct directions B1 [1]
- (ii) torque = force \times perpendicular distance (between forces) C1
 $= 1.6 \times 10^{-19} \times 5.0 \times 10^4 \times 2.8 \times 10^{-10} \times \sin 30$
 $= 1.1 \times 10^{-24} \text{ N m}$ A1 [2]

Q14.

- 6 (a) (i) $P = VI$ C1
 $60 = 12 \times I$
 $I = 5.0 \text{ A}$ A1 [2]
- (ii) either $V = IR$ or $P = I^2 R$ or $P = V^2 / R$ C1
either $12 = 5 \times R$ or $60 = 5^2 \times R$ or $60 = 12^2 / R$ M1
 $R = 2.4 \Omega$ A0 [2]
- (b) $R = \rho L / A$ C1
 $A = \pi \times (0.4 \times 10^{-3})^2 (= 5.03 \times 10^{-7})$ C1
 $L = (2.4 \times 5.03 \times 10^{-7}) / (1.0 \times 10^{-6})$
 $= 1.2 \text{ m}$ A1 [3]
- (c) resistance is halved M1
either current is doubled or power $\propto 1/R$ M1
power is doubled A1 [3]

Q15.



6 (a)	<i>either</i> $P \propto V^2$ <i>or</i> $P = V^2/R$	C1	
	reduction = $(230^2 - 220^2)/230^2$ = 8.5%	A1	[2]
(b) (i)	zero	A1	[1]
	(ii) 0.3(0)A	A1	[1]
(c) (i)	correct plots to within ± 1 mm	B1	[1]
	(ii) <u>reasonable line/curve</u> through points giving current as 0.12 A <i>allow</i> ± 0.005 A)	B1	[1]
	(iii) $V = IR$	C1	
	$V = 0.12 \times 5.0$ = 0.6(0)V	A1	[2]
(d)	circuit acts as a potential divider/current divides/current in AC not the same as current in BC	B1	
	resistance between A and C not equal to resistance between C and B	B1	
	or current in wire AC $\times R$ is not equal to current in wire BC $\times R$	B1	
	any 2 statements		[2]

Q16.

6 (a) (i)	movement/flow of charged particles	B1	[1]
	(ii) work done per unit charge (transferred)	B1	[1]
(b)	straight line through origin	B1	
	resistance = V/I , with values for V and I shown = 20Ω	M1 A0	[2]
	(using the gradient loses the last mark)		
(c) (i)	0.5A	A1	[1]
	(ii) <i>either</i> resistance of each resistor is 20Ω <i>or</i> total current = 0.8 A <i>either</i> combined resistance = 10Ω <i>or</i> $R = E/I = 10 \Omega$	C1 A1	[2]
(d) (i)	10V	A1	[1]
	(ii) power = EI = $10 \times 0.2 = 2.0$ W	C1 A1	[2]

Q17.

- 5 (a) (i) $I = 12 / (6 + 12)$
minimum current = 0.67 A C1
A1 [2]
- (ii) correct start and finish points M1
correct shape for curve with decreasing gradient A1 [2]
- (b) maximum current = 2.0 A A1
minimum current = 0 A1 [2]
- (c) (i) smooth curve starting at (0,0) with decreasing gradient M1
end section not horizontal A1 [2]
- (ii) full range of current / p.d. possible B1
or currents / p.d. down to zero [1]
or brightness ranging from off to full brightness

Q18.

- 5 (a) (i) energy converted from chemical to electrical when charge flows through cell
or round complete circuit B1
- (ii) (resistance of the cell) causing loss of voltage or energy loss in cell B1 [2]
- (b) (i) $E_B - E_A = I(R + r_B + r_A)$
 $12 - 3 = I(3.3 + 0.1 + 0.2)$
 $I = 2.5 \text{ A}$ C1
A1 [2]
- (ii) Power = $E \times I$
 $= 12 \times 2.5$
 $= 30 \text{ W}$ C1
A1 [2]
- (iii) $P = I^2 \times R$ or $P = V^2 / R$ or $P = VI$
 $= (2.5)^2 \times 3$ $= 9^2 / 3.6$ $= 9 \times 2.5$
 $= 22.5 \text{ Js}^{-1}$ C1
A1 [2]
- (c) power supplied from cell B is greater than energy lost per second in circuit B1 [1]

Q19.

- 5 (a) (i) Start from (0,0) and smooth curve in correct direction B1
Curve correct for end section never horizontal B1 [2]
- (ii) $R = V / I$ hence take co-ords of V and I from graph and calculate V / I B1 [1]
- (b) (i) each lamp in parallel has a greater p.d. / greater current M1
lamp hotter M1
resistance of lamps in parallel greater A1 [3]
- (ii) $P = V^2 / R$ or $P = VI$ and $V = IR$ C1
 $R = 144 / 50 = 2.88$ for each lamp C1
total $R = 1.44 \Omega$ A1 [3]

Q20.

- 4 (a) (i) $R = V^2 / P$ or $P = IV$ and $V = IR$
 $= (220)^2 / 2500$
 $= 19.4 \Omega$ (allow 2 s.f.) C1 A1 [2]
- (ii) $R = \rho l / A$ C1
 $l = [19.4 \times 2.0 \times 10^{-7}] / 1.1 \times 10^{-6}$ C1
 $= 3.53 \text{ m}$ (allow 2 s.f.) A1 [3]
- (b) (i) $P = 625, 620$ or 630 W A1 [1]
- (ii) R needs to be reduced C1
Either length $\frac{1}{4}$ of original length
or area $4\times$ greater
or diameter $2\times$ greater A1 [2]

Q21.

- 5 (a) (i) sum of e.m.f.'s = sum of p.d.'s around a loop/circuit B1 [1]
- (ii) energy B1 [1]
- (b) (i) $2.0 = I \times (4.0 + 2.5 + 0.5)$ C1
 $I = 0.286 \text{ A}$ (allow 2 s.f.) A1 [2]
(If total resistance is not 7Ω , 0/2 marks)
- (ii) $R = [0.90 / 1.0] \times 4 (= 3.6)$ C1
 $V = I R = 0.286 \times 3.6 = 1.03 \text{ V}$ A1 [2]
(If factor of 0.9 not used, then 0/2 marks)
- (iii) $E = 1.03 \text{ V}$ A1 [1]
- (iv) *either* no current through cell B
or p.d. across r is zero B1 [1]

Q22.

- 4 (a) total resistance = $20 \text{ (k}\Omega)$ C1
current = $12 / 20 \text{ (mA)}$ or potential divider formula C1
p.d. = $[12 / 20] \times 12 = 7.2 \text{ V}$ A1 [3]
- (b) parallel resistance = $3 \text{ (k}\Omega)$ C1
total resistance $8 + 3 = 11 \text{ (k}\Omega)$ C1
current = $12 / 11 \times 10^3 = 1.09 \times 10^{-3}$ or $1.1 \times 10^{-3} \text{ A}$ A1 [3]
- (c) (i) LDR resistance decreases M1
total resistance (of circuit) is less hence current increases A1 [2]
- (ii) resistance across XY is less M1
less proportion of 12 V across XY hence p.d. is less A1 [2]

Q23.

- 4 (a) electric field strength is the force per unit positive charge (acting on a stationary charge) B1 [1]
- (b) (i) $E = V / d$ C1
 $= 1200 / 14 \times 10^{-3}$
 $= 8.57 \times 10^4 \text{ V m}^{-1}$ A1 [2]
- (ii) $W = QV$ or $W = F \times d$ and therefore $W = E \times Q \times d$ C1
 $= 3.2 \times 10^{-19} \times 1200$
 $= 3.84 \times 10^{-16} \text{ J}$ A1 [2]
- (iii) $\Delta U = mgh$ C1
 $= 6.6 \times 10^{-27} \times 9.8 \times 14 \times 10^{-3}$
 $= 9.06 \times 10^{-28} \text{ J}$ A1 [2]
- (iv) $\Delta K = 3.84 \times 10^{-16} - \Delta U$
 $= 3.84 \times 10^{-16} \text{ J}$ A1 [1]
- (v) $K = \frac{1}{2}mv^2$ C1
 $v = [(2 \times 3.8 \times 10^{-16}) / 6.6 \times 10^{-27}]^{1/2}$
 $= 3.4 \times 10^5 \text{ ms}^{-1}$ A1 [2]

Q24.

- 5 (a) (i) sum of currents into a junction = sum of currents out of junction B1 [1]
- (ii) charge B1 [1]
- (b) (i) $\Sigma E = \Sigma IR$ C1
 $20 - 12 = 2.0(0.6 + R)$ (not used 3 resistors 0/2)
 $R = 3.4 \Omega$ A1 [2]
- (ii) $P = EI$ C1
 $= 20 \times 2$
 $= 40 \text{ W}$ A1 [2]
- (iii) $P = I^2 R$ C1
 $P = (2)^2 \times (0.1 + 0.5 + 3.4)$
 $= 16 \text{ W}$ A1 [2]
- (iv) efficiency = useful power / output power C1
 $24 / 40 = 0.6$ or $12 \times 2 / 20 \times 2$ or 60% A1 [2]

Q25.

- 6 (a) (i) chemical to electrical B1 [1]
(ii) electrical to thermal / heat or heat and light B1 [1]
- (b) (i) $(P_B =) EI$ or $I^2(R_1 + R_2)$ A1 [1]
(ii) $(P_R =) I^2R_1$ A1 [1]
- (c) $R = \rho l / A$ or clear from the following equation B1
ratio = $I^2R_1 / I^2R_2 = \frac{\rho l / \pi d^2}{\rho(2l) / \pi(2d)^2}$ or R_1 has 8× resistance of R_2 C1
= 8 or 8:1 A1 [3]
- (d) $P = V^2 / R$ or E^2 / R C1
(V or E the same) hence ratio is 1/8 or 1:8 = 0.125 (allow ecf from (c)) A1 [2]

Q26.

- 6 (a) charge = current × time B1 [1]
- (b) (i) $P = V^2 / R$ C1
= $(240)^2 / 18 = 3200\text{W}$ A1 [2]
- (ii) $I = V / R = 240 / 18 = 13.3\text{A}$ A1 [1]
- (iii) charge = $It = 13.3 \times 2.6 \times 10^6$ C1
= $3.47 \times 10^7\text{C}$ A1 [2]
- (iv) number of electrons = $3.47 \times 10^7 / 1.6 \times 10^{-19}$ (= 2.17×10^{26}) C1
number of electrons per second = $2.17 \times 10^{26} / 2.6 \times 10^6 = 8.35 \times 10^{19}$ A1 [2]

Q27.

- 6 (a) p.d. = $\frac{\text{work done} / \text{energy transformed}}{\text{charge}}$ (from electrical to other forms) B1 [1]
- (b) (i) maximum 20V A1 [1]
(ii) minimum = $(600 / 1000) \times 20$ C1
= 12V A1 [2]
- (c) (i) use of 1.2kΩ M1
 $1/1200 + 1/600 = 1/R$, $R = 400\Omega$ A1 [2]
- (ii) total parallel resistance ($R_2 + \text{LDR}$) is less than R_2 M1
(minimum) p.d. is reduced A1 [2]

Q28.

- 6 (a) (i) arrow in upward direction, foot near P B1
(ii) curved path consistent with (i) between plates B1
then straight (with no kink at change-over) B1 [3]
- (b) $E = V/d$ C1
 $= 400 / (0.8 \times 10^{-2})$
 $= 5.0 \times 10^4 \text{ V m}^{-1}$ (allow 1 sig fig) A1 [2]
- (c) (i) $F = Eq$ C1
 $= 5.0 \times 10^4 \times 1.6 \times 10^{-19}$
 $= 8.0 \times 10^{-15} \text{ N}$ (allow 1 sig fig and e.c.f.) A1
- (ii) $a = F/m$ C1
 $= (8.0 \times 10^{-15}) / (9.1 \times 10^{-31})$
 $= 8.8 \times 10^{15} \text{ m s}^{-2}$ (allow 1 sig fig and e.c.f.) A1 [4]
- (d) because F_E is normal to horizontal motion M1
no effect A1 [2]

Q29.

- 7 (a) (i) e.m.f. = energy / charge C1
 $= (1.6 \times 10^5) / (1.8 \times 10^4)$
 $= 8.9 \text{ V}$ A1
- (ii) current = $\Delta Q / \Delta t$ C1
 $= (1.80 \times 10^4) / (1.3 \times 10^5)$
 $= 0.14 \text{ A}$ A1 [4]
- (b) (i) energy $\propto R$ (or formula) C1
energy = $(15 / 45) \times 1.14 \times 10^5$ C1
 $= 3.7 \times 10^4 \text{ J}$ A1
- (ii) energy dissipated in internal resistance (of battery) B1 [4]
OR in extra resistance in circuit


Q30.

- 5 (a) (i) arrow from B towards A..... B1
- (ii) $E = V/d$
 $= 450/(9.0 \times 10^{-2})$ C1
 $= 5.0 \times 10^3 \text{ N C}^{-1}$ (accept 1 sig. fig) A1 [3]
- (b) (i) energy = qV or Eqd C1
 $= 1.6 \times 10^{-19} \times 450$ A1
 $= 7.2 \times 10^{-17} \text{ J}$ A0
- (ii) $E_k = \frac{1}{2}mv^2$
 $7.2 \times 10^{-17} = \frac{1}{2} \times 9.1 \times 10^{-31} \times v^2$ C1
 $v = 1.26 \times 10^7 \text{ m s}^{-1}$ A1 [4]
- (c) line from origin, curved in correct direction but not 'level out' B1 [1]

Q31.

- 7 (a) (i) $P = Vi$ C1
 $1200 = 240 \times i$ M1
 $i = 5.0 \text{ A}$ A0
- (ii) $V = iR$
 $240 = 5.0 \times R$ C1
 $R = 48\Omega$ A1 [4]
- (b) (i) p.d. = $(5.0 \times 4.0 =) 20 \text{ V}$ A1
- (ii) mains voltage = $(240 + 20 =) 260 \text{ V}$ A1
- (iii) $P = (20 \times 5.0 =) 100 \text{ W}$ A1 [3]
- (c) power input = $1200 + 100 = 1300 \text{ W}$ C1
efficiency = $1200/1300 = 0.92$ A1 [2]

Q32.

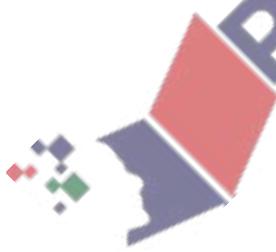

- 6 (a) (i) resistance is ratio V/I (at a point) B1
either gradient increases or I increases more rapidly than V B1 [2]
(If states $R =$ reciprocal of gradient, then 0/2 marks here)
- (ii) current = 2.00 mA C1
 resistance = 2 000 Ω A1 [2]
- (b) (i) straight line from origin M1
 passing through (6.0 V, 4.0 mA) (allow $\frac{1}{2}$ square tolerance) A1 [2]
- (ii) individual currents are 0.75 mA and 1/33 mA C1
 current in battery = 2.1 mA A1 [2]
(allow argument in terms of $P = I^2R$ or IV)
- (c) same current in R and in C M1
 p.d. across C is larger than that across R M1
 so since power = VI , greater in C A1 [3]
(allow argument in terms of $P = I^2R$ or IV)

Q33.

- 6 (a) force must be upwards (on positive charge)
 so plate Y is positive M1
A1 [2]
- (b) (i) $E = V/d$ C1
 $= 630/(0.75 \times 10^{-2})$
 $= 8.4 \times 10^4 \text{ N C}^{-1}$ A1 [2]
- (ii) $qE = mg$ C1
 $q = (9.6 \times 10^{-15} \times 9.8) / (8.4 \times 10^4)$ C1
 $= 1.12 \times 10^{-18} \text{ C}$ A1 [3]

Q34.

- 7 (a) *either* $V = E R_1 / (R_1 + R_2)$ *or* $I = E / (R_1 + R_2)$ C1
 $= \frac{1800}{3000} \times 4.50$ $V = \frac{1800}{3000} \times 4.50$ M1
 $= 2.70 \text{ V}$ $= 2.70 \text{ V}$ A0 [2]
- (b) (i) for a wire, $V = I \times (\rho L/A)$ M1
 I, ρ and A are constant A1
 so $V \propto L$ A0 [2]

- (ii) 1 2.70 V A1 [1]
 2 $\frac{L}{100} = \frac{2.70}{4.50}$ C1
 $L = 60.0$ cm A1 [2]
 (iii) thermistor resistance decreases as temperature rises M1
 so QM is shorter A1 [2]

Q35.

- 7 (a) both measure (energy / work) / charge B1
 for e.m.f., transfer of chemical energy to electrical energy B1
 for p.d., transfer of electrical energy to thermal energy / other forms B1 [3]
 (b) (i) $I_1 + I_2 = I_3$ B1 [1]
 (ii) 1. $E_2 = I_2 R_2 + I_3 R_3$ B1 [1]
 2. $E_1 - E_2 = I_1 R_1 - I_2 R_2$ B1 [1]

Q36.

- 6 (a) power = VI C1
 current = $10.5 \times 103 / 230$ M1
 $= 45.7$ A A0 [2]
 (b) (i) p.d. across cable = 5.0 V C1
 $R = 5.0 / 46$ C1
 $= 0.11 \Omega$ A1 [3]
 (ii) $R = \rho L / A$ C1
 $0.11 = (1.8 \times 10^{-8} \times 16 \times 2) / A$ C1
 $A = 5.3 \times 10^{-6} \text{ m}^2$ A1 [3]
 (wires in parallel, not series, allow max 1/3 marks)
 (c) (i) either power = V^2 / R or power $\propto V^2$ C1
 ratio = $(210 / 230)^2 = 0.83$ A1 [2]
 (ii) resistance of cable is greater M1
 greater power loss/fire hazard/insulation may melt
 wire may melt/cable gets hot A1 [2]

Q37.

- 4 (a) (i) either force = $e \times (V / d)$ or $E = V/d$ C1
 $= 1.6 \times 10^{-19} \times (250 / 7.6 \times 10^{-3})$ C1
 $= 5.3 \times 10^{-15} \text{ N}$ A1 [3]
 (ii) either $\Delta E_k = eV$ or $\Delta E_k = Fd$ C1
 $= 1.6 \times 10^{-19} \times 250$ M1
 $= 4.0 \times 10^{-17} \text{ J}$ $= 5.3 \times 10^{-15} \times 7.6 \times 10^{-3}$ A0 [2]
 (allow full credit for correct working via calculation of a and v)

- (iii) either $\Delta E_K = \frac{1}{2}mv^2$
 $4.0 \times 10^{-17} = \frac{1}{2} \times 9.1 \times 10^{-31} \times v^2$ C1
 $v = 9.4 \times 10^6 \text{ m s}^{-1}$ A1 [2]
- or $v^2 = 2as$ and $a = F/m$
 $v^2 = (2 \times 5.3 \times 10^{-15} \times 7.6 \times 10^{-3}) / (9.11 \times 10^{-31})$ (C1)
 $v = 9.4 \times 10^6 \text{ m s}^{-1}$ (A1)
- (b) speed depends on (electric) potential difference M2
(If states ΔE_K does not depend on uniformity of field, then
award 1 mark, treated as an M mark)
 so speed always the same A1 [3]

Q38.

- 7 (a) either $V = IP$ B1
 current in circuit = $E / (P + Q)$ B1
 hence $V = EP / (P + Q)$ A0 [2]
- or current is the same throughout the circuit (M1)
 $V/P = E / (P + Q)$ (A1)
 hence $V = EP / (P + Q)$ (A0)
- (b) (i) (as temperature rises), resistance of (thermistor) decreases M1
 either resistance of parallel combination decreases
 or p.d. across 5 k Ω resistor / thermistor decreases M1
 p.d. across 2000 Ω resistor / voltmeter reading increases A1 [3]
- (ii) if R is the resistance of the parallel combination,
 either $3.6 = (2 \times 6) / (2 + R)$ or current in 2 k Ω resistor = 1.8 mA C1
 $R = 1.33 \text{ k}\Omega$ current in 5 k Ω resistor = 0.48 mA C1
 $\frac{1}{1.33} = \frac{1}{5} + \frac{1}{T}$ current in thermistor = 1.32 mA C1
 $T = 1.82 \text{ k}\Omega$ $T = 2.4 / 1.32 = 1.82 \text{ k}\Omega$ A1 [4]

Q39.

- 6 (a) energy transferred from source / changed from some form to electrical M1
 per unit charge (to drive charge round a complete circuit) A1 [2]
- (b) and power in $R = I^2X$ M1
 $E = I(X + r)$ M1
 power in cell = EI and algebra clear leading to ratio = $X / (X + r)$ A1 [3]

- (c) (i) 1.4 W A1
 0.40 Ω (allow $\pm 0.05 \Omega$) A1 [2]
- (ii) current in circuit = $\sqrt{1.4/0.4} = 1.87 \text{ A}$ C1
 1.5 = 1.87 ($r + 0.40$) C1
 $r = 0.40 \Omega$ A1 [3]
- (d) either less power lost / energy wasted / lost B1 [1]
 or greater efficiency (of energy transfer)

[Total: 11]

Q40.

- 6 (a) total resistance in series = $2R$ M1
 total resistance in parallel = $\frac{1}{2}R$ A0 [1]
 ratio is $2R / \frac{1}{2}R = 4$ (allow mark if clear numbers in the ratio)
- (b) at 1.5 V, current is 0.10 A C1
 resistance = $V/I = \frac{1.5}{0.1}$ A1 [2]
 = 15 Ω
 (use of tangent or any other current scores no marks)

(c)

	p.d. across each lamp / V	resistance of each lamp / Ω	combined resistance / Ω
series	1.5	15	30
parallel	3.0	20	10

- column 1 A1
 columns 2 and 3: max 3 marks with -1 mark for each error or omission A3 [4]

- (d) (i) ratio is 3(allow e.c.f.) A1 [1]
- (ii) resistance increases as potential difference increases B1
 increasing p.d. increases current B1
 current increases non-linearly so resistance increases B1 [3]

[Total: 11]


Q41.

- 6 (a) (i) either $P = V^2 / R$ or $P = VI$ and $V = IR$
 $R = 4.0 \Omega$ C1
A1 [2]
- (ii) sketch vertical axis labelled appropriately B1
(staight) line from origin then curved in correct direction B1
line passes through 12 V, 3.0 A B1 [3]
- (b) (i) 2.0 kW A1 [1]
- (ii) 0.5 kW A1 [1]
- (iii) total resistance = $3R / 2$ C1
power = 0.67 kW A1 [2]

Q42.

- 6 (a) (i) at 22.5 °C, $R_T = 1600 \Omega$ or 1.6 k Ω C1
total resistance = 800 Ω A1 [2]
- (ii) either use of potential divider formula or current = $9 / 2000$ (4.5 mA) C1
 $V = (0.8/2.0) \times 9$ $V = (9/2000) \times 800$
= 3.6V = 3.6V A1 [2]
- (b) (i) total resistance = $4/5 \times 1200$ C1
= 960 Ω A1 [2]
- (ii) for parallel combination, $1/960 = 1/1600 + 1/R_T$ C1
 $R_T = 2400 \Omega$ / 2.4 k Ω A1 [2]
temperature = 11 °C
- (c) e.g. only small part of scale used / small sensitivity B1
non-linear B1 [2]
(any two sensible suggestions, 1 each, max 2)

Q43.

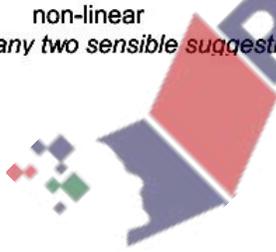

- 7 (a) (i) path: reasonable curve upwards between plates
straight and at a tangent to the curve beyond the plates B1
B1 [2]
- (ii) 1. $(F =) Eq$ B1 [1]
2. $(t =) L/v$ B1 [1]
- (b) (i) total momentum of a system remains constant or total momentum of a system before a collision equals total momentum after collision provided no external force acts on the system M1
A1 [2]
(do not accept 'conserved' but otherwise correct statement gets 1/2)
- (ii) $(\Delta p =) EqL/v$ allow ecf from (a)(ii) B1 [1]
- (iii) either charged particle is not an isolated system M1
so law does not apply A1 [2]
or system is particle and 'plates' (M1)
equal and opposite Δp on plates / so law applies (A1)

Q44.

- 8 (a) (i) either $P = V^2 / R$ or $I = 1200 / 230$ or 5.22 C1
 $R = 230^2 / 1200$ or $R = (230 \times 230) / 1200$ M1
 $= 44.1 \Omega$ or $R = 230 / 5.22$ A0 [2]
 $= 44.1 \Omega$
- (ii) $R = \rho L / A$ C1
 $= (1.7 \times 10^{-8} \times 9.2 \times 2) / (\pi \times \{0.45 \times 10^{-3}\}^2)$ M1
 $= 0.492 \Omega$ A0 [2]
- (b) current = $230 / 44.6$ C1
power = $(230 / 44.6)^2 \times 44.1$ C1
 $= 1170 \text{ W}$ A1 [3]
(allow full credit for solution based on potential divider)
- (c) e.g. less power dissipated in the heater / smaller p.d. across heater / more power loss in cable / current lower B1
cable becomes heated / melts B1 [2]
(any two sensible suggestions, 1 each, max 2)

Q45.

- 5 (a) ohm = volt / ampere B1 [1]
- (b) $\rho = RA / l$ or unit is Ωm C1
 units: $VA^{-1} m^2 m^{-1} = NmC^{-1} A^{-1} m^2 m^{-1}$ C1
 $= kgm^2 s^{-2} A^{-1} s^{-1} A^{-1} m^2 m^{-1}$
 $= kgm^3 s^{-3} A^{-2}$ A1 [3]
- (c) (i) $\rho = [3.4 \times 1.3 \times 10^{-7}] / 0.9$ C1
 $= 4.9 \times 10^{-7} (\Omega m)$ A1 [2]
- (ii) max = 2.0 V A1
 min = $2 \times (3.4 / 1503.4) = 4.5 \times 10^{-3} V$ A1 [2]
- (iii) $P = V^2 / R$ or $P = VI$ and $V = IR$ C1
 $= (2)^2 / 3.4$
 $= 1.18$ (allow 1.2) W A1 [2]
- (d) (i) power in Q is zero when $R = 0$ B1 [1]
- (ii) power in Q = 0 / tends to zero as $R =$ infinity B1 [1]

Q46.

- 4 (a) electric field strength = force / positive charge B1 [1]
- (b) (i) at least three equally spaced parallel vertical lines B1
 direction down B1 [2]
- (ii) $E = 1500 / 20 \times 10^{-3} = 75000 V m^{-1}$ A1 [1]
- (iii) $F = qE$ C1
 $(W = mg \text{ and } qE = mg)$ C1
 $q = mg / E = 5 \times 10^{-15} \times 9.81 / 75000$
 $= 6.5 \times 10^{-19} C$ A1
 negative charge A1 [4]
- (iv) $F > mg$ or F now greater B1
 drop will move upwards B1 [2]

Q47.

- 5 (a) (i) $I_1 + I_3 = I_2$ A1 [1]
- (ii) $E_1 = \frac{I_2 R_2}{2} + \frac{I_1 R_2}{2} + I_1 R_1 + I_1 r_1$ A1 [1]
- (iii) $E_1 - E_2$ B1
 $= -I_3 r_2 + I_1 (R_1 + r_1 + R_2 / 2)$ B1 [2]
- (b) p.d. across BJ of wire changes / resistance of BJ changes B1
 there is a difference in p.d. across wire and p.d. across cell E_2 B1 [2]

Q48.

- 4 (a) p.d. = $\frac{\text{energy transformed from electrical to other forms}}{\text{unit charge}}$ B1
- e.m.f. = $\frac{\text{energy transformed from other forms to electrical}}{\text{unit charge}}$ B1 [2]
- (b) (i) sum of e.m.f.s (in a closed circuit) = sum of potential differences B1 [1]
- (ii) $4.4 - 2.1 = I \times (1.8 + 5.5 + 2.3)$ M1
 $I = 0.24 \text{ A}$ A1 [2]
- (iii) arrow (labelled) I shown anticlockwise A1 [1]
- (iv) 1. $V = I \times R = 0.24 \times 5.5 = 1.3(2)\text{V}$ A1 [1]
2. $V_A = 4.4 - (I \times 2.3) = 3.8(5)\text{V}$ A1 [1]
3. either $V_B = 2.1 + (I \times 1.8)$ or $V_B = 3.8 - 1.3$
 $= 2.5(3)\text{V}$ C1
A1 [2]

Q49.

- 2 (a) resistance = potential difference / current B1 [1]
- (b) (i) metal wire in series with power supply and ammeter B1
voltmeter in parallel with metal wire B1
rheostat in series with power supply or potential divider arrangement B1 [3]
or variable power supply
- (ii) 1. intercept on graph B1 [1]
2. scatter of readings about the best fit line B1 [1]
- (iii) correction for zero error explained B1
use of V and corrected I values from graph C1
resistance = $V/I = 22.(2)\Omega$ [e.g. $4.0 / 0.18$] A1 [3]
- (c) $R = 6.8 / 0.64 = 10.625$ C1
- $\%R = \%V + \%I$
 $= (0.1 / 6.8) \times 100 + (0.01 / 0.64) \times 100$ C1
 $= 1.47\% + 1.56\%$
- $\Delta R = 0.0303 \times 10.625 = 0.32\Omega$
 $R = 10.6 \pm 0.3 \Omega$ A1 [3]

Q50.

- 5 (a) (i) $I_1 = I_2 + I_3$ B1 [1]
- (ii) $I = V / R$ or $I_2 = 12 / 10$ (= 1.2 A) C1
 $R = [1/6 + 1 / 10]^{-1}$ [total $R = 3.75 \Omega$] or $I_3 = 12 / 6$ (= 2.0 A) C1
 $I_1 = 12 / 3.75 = 3.2 \text{ A}$ or $I_1 = 1.2 + 2.0 = 3.2 \text{ A}$ A1 [3]
- (iii) power = VI or I^2R or V^2 / R C1
- $x = \frac{\text{power in wire}}{\text{power in series resistors}} = \frac{I_2^2 R_w}{I_3^2 R_s}$ or $\frac{V_2}{V_3}$ or $\frac{V^2 / R_w}{V^2 / R_s}$ C1
- $x = 12 \times 1.2 / 12 \times 2.0 = 0.6(0)$ allow 3 / 5 or 3:5 A1 [3]
- (b) p.d. BC: $12 - 12 \times 0.4 = 7.2 \text{ (V)}$ / p.d. AC = 4.8(V) C1
 p.d. BD: $12 - 12 \times 4 / 6 = 4.0 \text{ (V)}$ / p.d. AD = 8.0(V) C1
 p.d. = 3.2V A1 [3]

Q51.

- 4 (a) e.m.f. = chemical energy to electrical energy M1
 p.d. = electrical energy to thermal energy M1
 idea of per unit charge A1 [3]
- (b) $E = I(R+r)$ or $I = E / (R+r)$ (any subject) B1 [1]
- (c) (i) $E = 5.8 \text{ V}$ B1 [1]
- (ii) evidence of gradient calculation or calculation with values from graph
 e.g. $5.8 = 4 + 1.0 \times r$ C1
 $r = 1.8 \Omega$ A1 [2]
- (d) (i) $P = VI$ C1
 $P = 2.9 \times 1.6 = 4.6$ (4.64)W A1 [2]
- (ii) power from battery = $1.6 \times 5.8 = 9.28$ or efficiency = VI / EI C1
 efficiency = $(4.64 / 9.28) \times 100 = 50 \%$ or $(2.9 / 5.8) \times 100 = 50\%$ A1 [2]

Q52.

- 6 (a) p.d. = work (done) / charge OR energy transferred from (electrical to other forms) / (unit) charge B1 [1]
- (b) (i) $R = \rho l / A$ C1
 $\rho = 18 \times 10^{-9}$ C1
 $R = (18 \times 10^{-9} \times 75) / 2.5 \times 10^{-6} = 0.54 \Omega$ A1 [3]
- (ii) $V = IR$ C1
 $R = 38 + (2 \times 0.54)$ C1
 $I = 240 / 39.08 = 6.1$ (6.14) A A1 [3]

(iii) $P = I^2 R$ or $P = VI$ and $V = IR$ or $P = V^2/R$ and $V = IR$ C1
 $= (6.14)^2 \times 2 \times 0.54$ C1
 $= 41 (40.7) \text{ W}$ A1 [3]

- (c) area of wire is less (1/5) hence resistance greater ($\times 5$) M1
 OR R is $\propto 1/A$ therefore R is greater
 p.d. across wires greater so power loss in cables increases A1 [2]

Q53.

- 6 (a) e.m.f. = total energy available (per unit charge) B1
 some (of the available energy) is used/lost/wasted/given out in the internal
 resistance of the battery (hence p.d. available less than e.m.f.) B1 [2]
- (b) (i) $V = IR$ C1
 $I = 6.9 / 5.0 = 1.4 (1.38) \text{ A}$ A1 [2]
- (ii) $r = \text{lost volts} / \text{current}$ C1
 $= (9 - 6.9) / 1.38 = 1.5(2) \Omega$ A1 [2]
- (c) (i) $P = EI$ (not $P = VI$ if only this line given or 9 V not used in second line) C1
 $= 9 \times 1.38 = 12 (12.4) \text{ W}$ A1 [2]
- (ii) efficiency = output power / total power C1
 $= VI / EI = 6.9 / 9$ or $(9.52) / (12.4) = 0.767 / 76.7\%$ A1 [2]

Q54.

- 7 (a) (i) six vertical lines from plate to plate equally spaced across plates B1
 [only allow if greatest to least spacing is < 1.3 , condone slight curving on the
 two edges. There must be no area between the plates where an additional
 line(s) could be added.]
 arrow downwards on at least one line B1 [2]
- (ii) $E = V/d$ C1
 $= 1200 / 40 \times 10^{-3} = 3.0 \times 10^4 \text{ Vm}^{-1}$ (allow 1 s.f.) A1 [2]
- (b) (i) $F = Ee$ C1
 $= 3 \times 10^4 \times 1.6 \times 10^{-19} = 4.8 \times 10^{-15} \text{ N}$ A1 [2]
- (ii) couple = $F \times \text{separation of charges}$ C1
 $= 4.8 \times 10^{-15} \times 15 \times 10^{-3} = 7.2 \times 10^{-17}$ A1
 unit: N m or unit consistent with unit used for the separation B1 [3]
- (iii) A at top/next to +ve plate B at bottom/next to -ve plate vertically aligned M1
 [could be shown on the diagram]
 forces are equal and opposite in same line / no resultant force and no
 resultant torque A1 [2]