



General Certificate of Secondary Education  
2016

Centre Number

--	--	--	--	--	--

Candidate Number

--	--	--	--	--	--

## Technology and Design

Unit 2:

Systems and Control

Element 1: Electronic and  
Microelectronic Control Systems

MV18

[GTD21]

**MONDAY 6 JUNE, AFTERNOON**

### Time

1 hour, plus your additional time allowance.

### Instructions to Candidates

Write your Centre Number and Candidate Number in the spaces provided at the top of this page.

**You must answer the questions in the spaces provided.**

Questions which require drawing or sketching should be completed using an H.B. pencil.

All other questions must be completed using blue or black ink only.  
Answer **all** questions.

### Information for Candidates

The total mark for this paper is 80.

Figures in brackets printed at the end of each question indicate the marks awarded to each question or part question.

**Blank Page**


# Formulae for GCSE Technology and Design

You should use, where appropriate, the formulae given below when answering questions which include calculations.

**1** Potential Difference = current  $\times$  resistance ( $V = I \times R$ )

**2** For potential divider
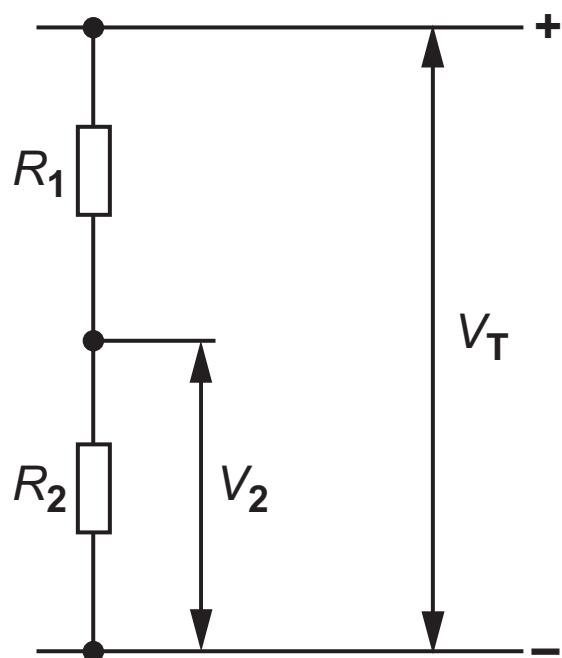
$$V_2 = \frac{R_2}{R_1 + R_2} \times V_T$$



**3** Series Resistors

$$R_T = R_1 + R_2 + R_3 \text{ etc}$$

Parallel Resistors

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{or} \quad R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$

**4** Time Constant  $T = R \times C$

Answer **all** questions


1 (a) (i) Ohm's Law can be expressed in three different ways.  
Complete the formula in each case below. [3 marks]

$$V =$$


$$I =$$

$$R =$$

(ii) Use Ohm's Law to calculate the current which goes through the resistor shown in **Fig. 1** and the resistor shown in **Fig. 2**. [2 marks for each current]

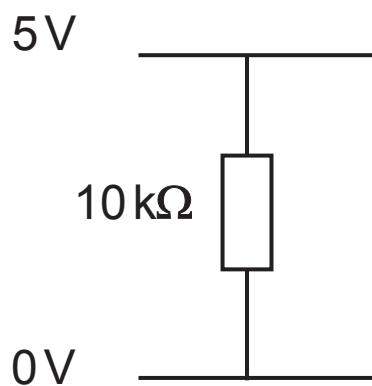

**Fig. 1**

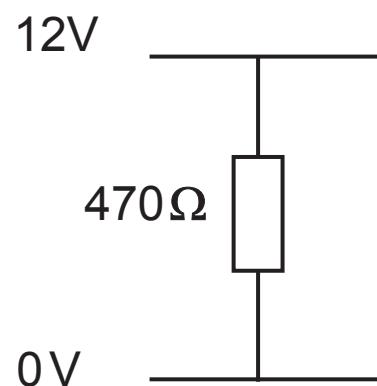

**Fig. 2**

**Current Fig. 1** \_\_\_\_\_


**Current Fig. 2** \_\_\_\_\_

(iii) State the function of an ammeter and a voltmeter when used in a circuit. [1 mark for each]


Ammeter \_\_\_\_\_

Voltmeter \_\_\_\_\_

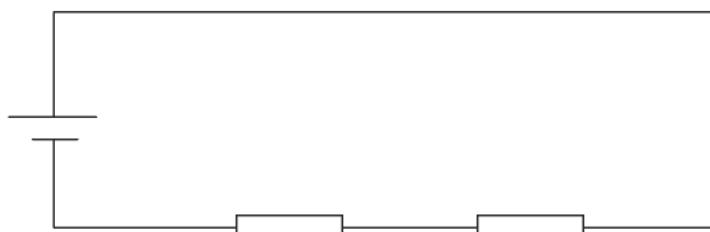
(iv) Using the correct electronic symbol show how an ammeter could be connected in the circuit below. [2 marks]



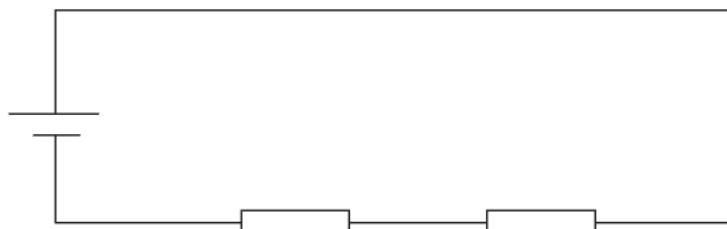(v) Using the correct electronic symbol show how a voltmeter could be connected in the circuit below. [2 marks]



(b) (i) Name the component labelled B in Fig. 3 below.  
[1 mark]

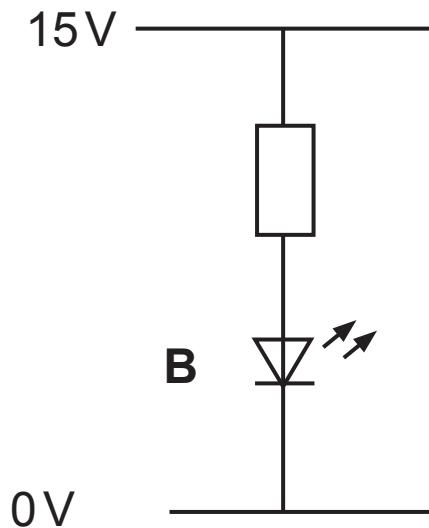

**Fig. 3**

---


(ii) If component B is rated at 2V, 20mA, calculate in the space below the minimum value for the resistor in Fig. 3. [3 marks]

(iii) State the tolerance for the E12 series of resistors.  
[1 mark]

Tolerance \_\_\_\_\_

---

(c) (i) Name the electronic component represented by the symbol in **Fig. 4**. [1 mark]

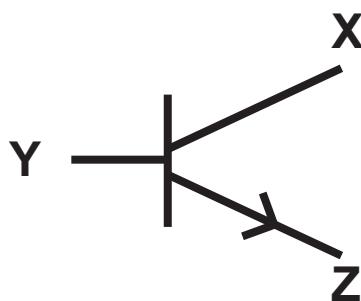

**Fig. 4**

---

(ii) Name each part of the symbol labelled at **X**, **Y** and **Z**. [1 mark for each part]

Point **X** \_\_\_\_\_

Point **Y** \_\_\_\_\_


Point **Z** \_\_\_\_\_

(iii) Explain how the component should operate or respond when connected in a circuit. [2 marks]

---

---

(d) A circuit is shown in **Fig. 5**. The power supply required is 9V. Resistor R1 has a value of  $1.8\text{ k}\Omega$  and resistor R2 has a value of  $2.2\text{ k}\Omega$ .

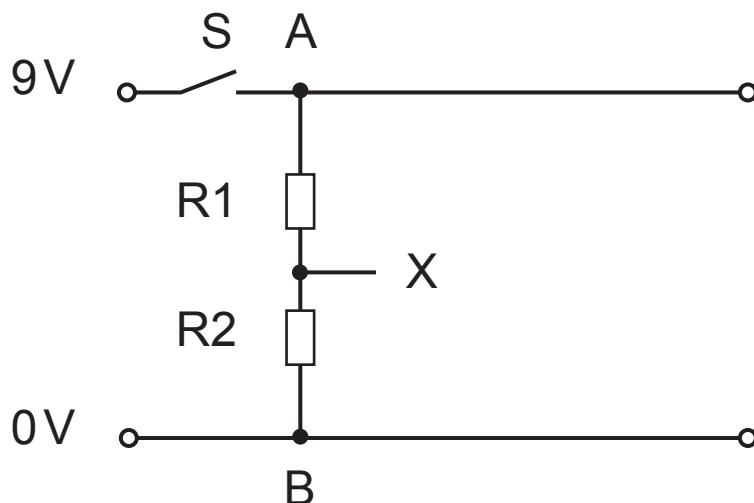

**Fig. 5**

A number of 1.5V batteries are required to provide the 9V supply for the circuit.

(i) State how they should be connected together.  
[1 mark]

\_\_\_\_\_

(ii) State the number of batteries required. [1 mark]

\_\_\_\_\_

(iii) Name that part of the circuit connected between A and B. [1 mark]

\_\_\_\_\_

(iv) Calculate the output voltage at point X when the switch S is pressed. [4 marks]

Output Voltage \_\_\_\_\_

(e) Fig. 6 shows a circuit under construction.

(i) Complete the circuit to enable a buzzer to operate when required. Your solution should include the symbol shown in Fig. 4, a buzzer symbol, a diode symbol and the one additional component symbol needed. [6 marks]

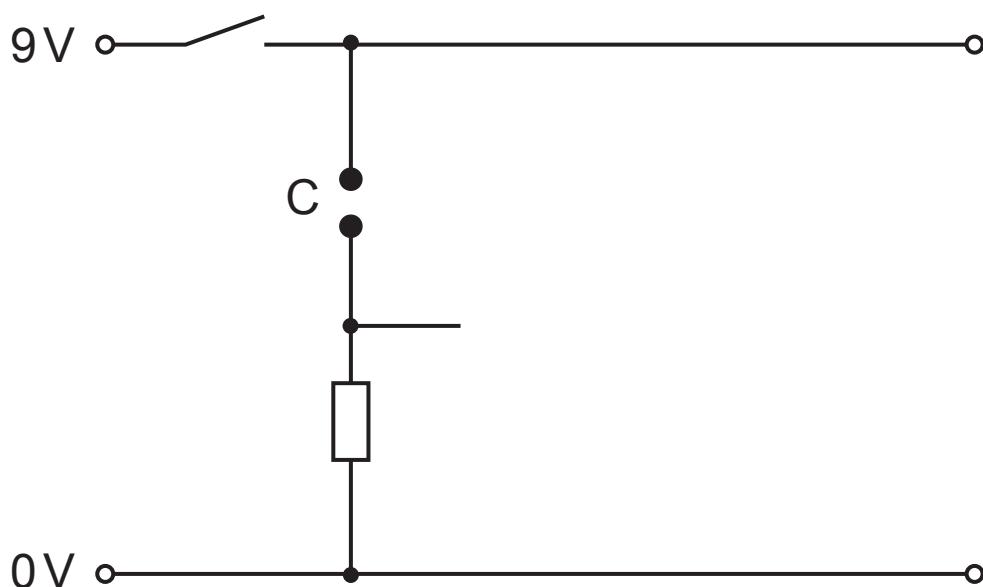


Fig. 6

(ii) Name the component symbol labelled C in Fig. 6. [1 mark]

---

(iii) Briefly explain how the buzzer is activated in the completed circuit. [2 marks]

---

---

---

2 (a) Fig. 7 shows an incomplete PIC circuit. Complete the circuit as follows: [5 marks]

- add the power connections to the PIC;
- add the appropriate component symbols so that the PIC may control the motor.

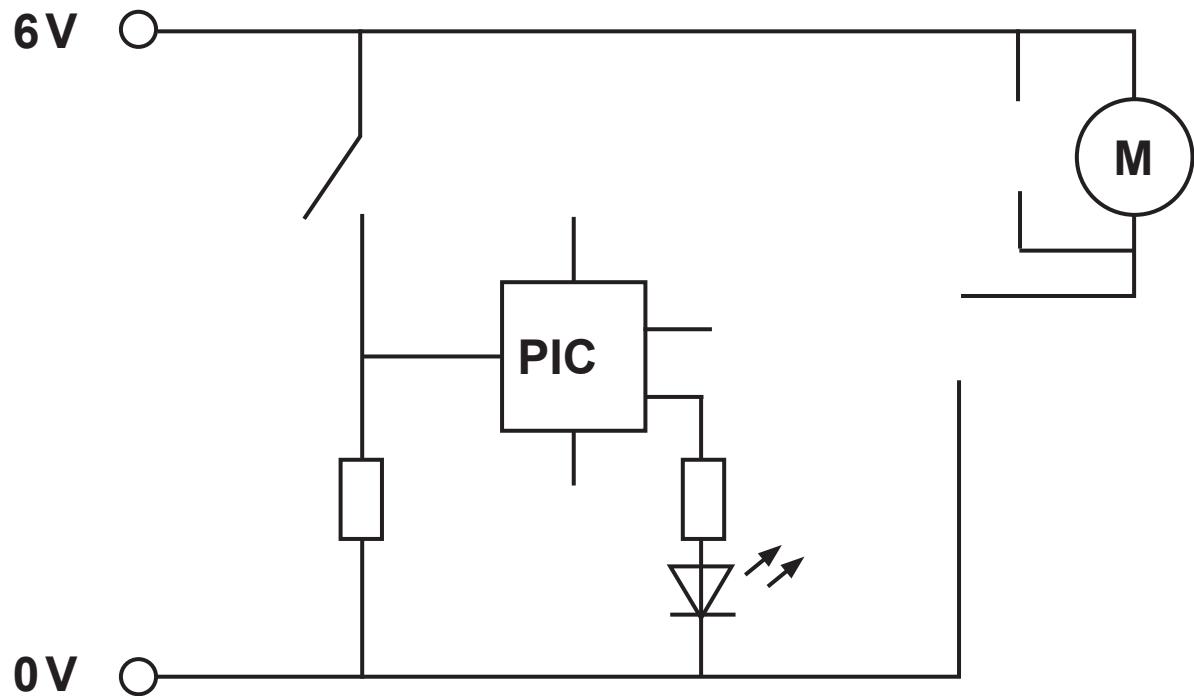


Fig. 7

**(b) (i)** What **two** digital numbers are used in Bit Patterns?  
[1 mark]

---


**(ii)** What is a main function of a Bit Pattern when used  
in a flow chart? [2 marks]

---


---

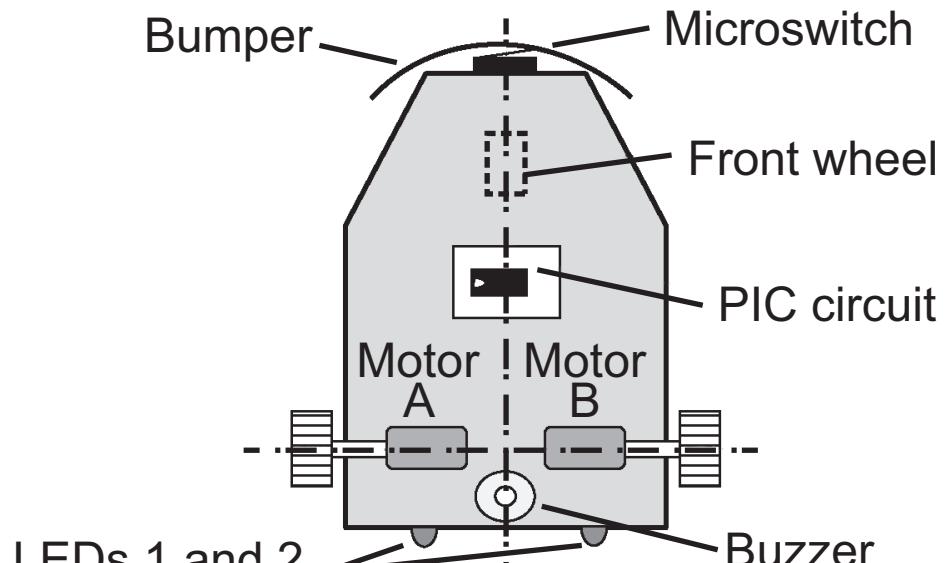(c) **Fig. 8** opposite shows two views of a motorised buggy. The buggy is to be programmed using a Microcontroller (PIC). It is to travel in a set routine within a wooden box as shown in **Fig. 9** on page 14.

The slide switch is connected as an input to the PIC circuit. The “Power on” LED is also controlled by the PIC. The buggy has two small motors attached to the rear wheels to enable it to move and a front wheel for stability. The buggy is fitted with a microswitch which is attached to the front bumper to detect if the buggy comes into contact with the sides of the box. When this happens, the buggy will stop. Then LEDs 1 and 2 will flash and the buzzer will sound. The buggy will then reverse and turn to the right through 90° and move forward again. This process is continued until the slide switch is turned off.




**Plan View (without body)**

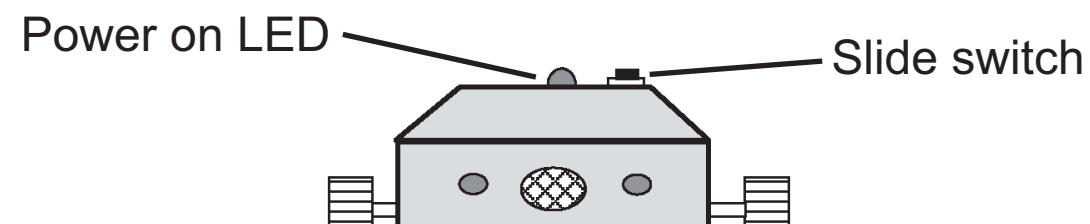

**Rear View (with body)**

**Fig. 8**

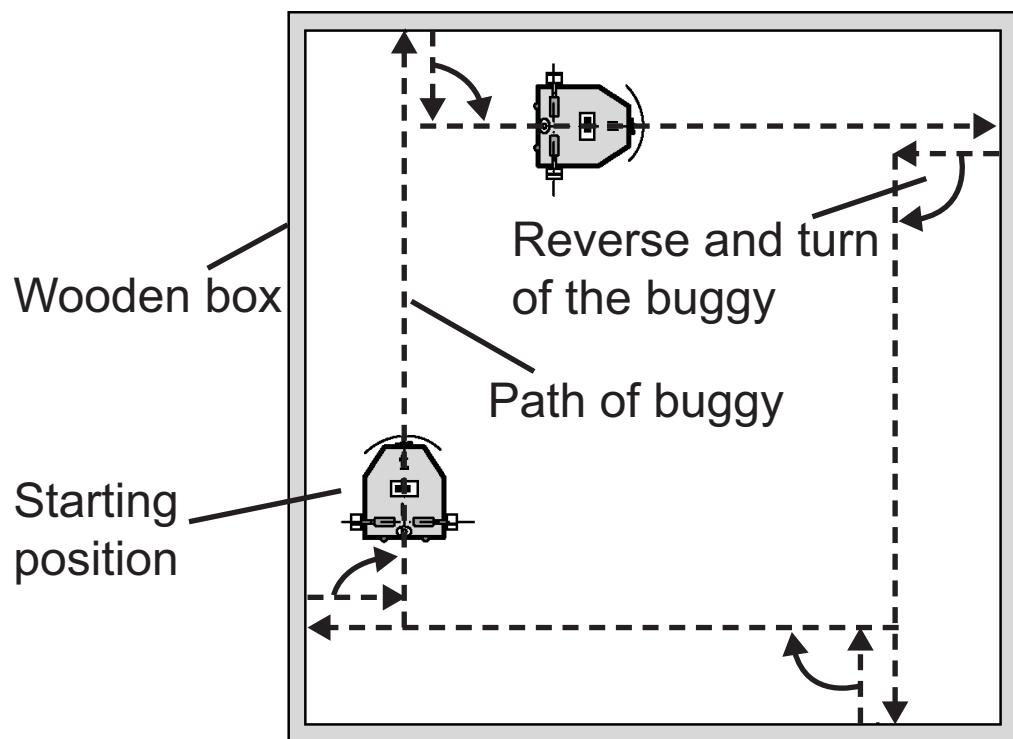


**Fig. 9**

Complete a series of flow charts for the buggy using the correct flow chart symbols.

(i) Complete the flow chart in **Fig. 10** to represent the **Forward** macro as follows: [4 marks]

The two motors **A** and **B** will come on and move the buggy forward. When the microswitch attached to the bumper is operated the two motors will stop and end the macro.

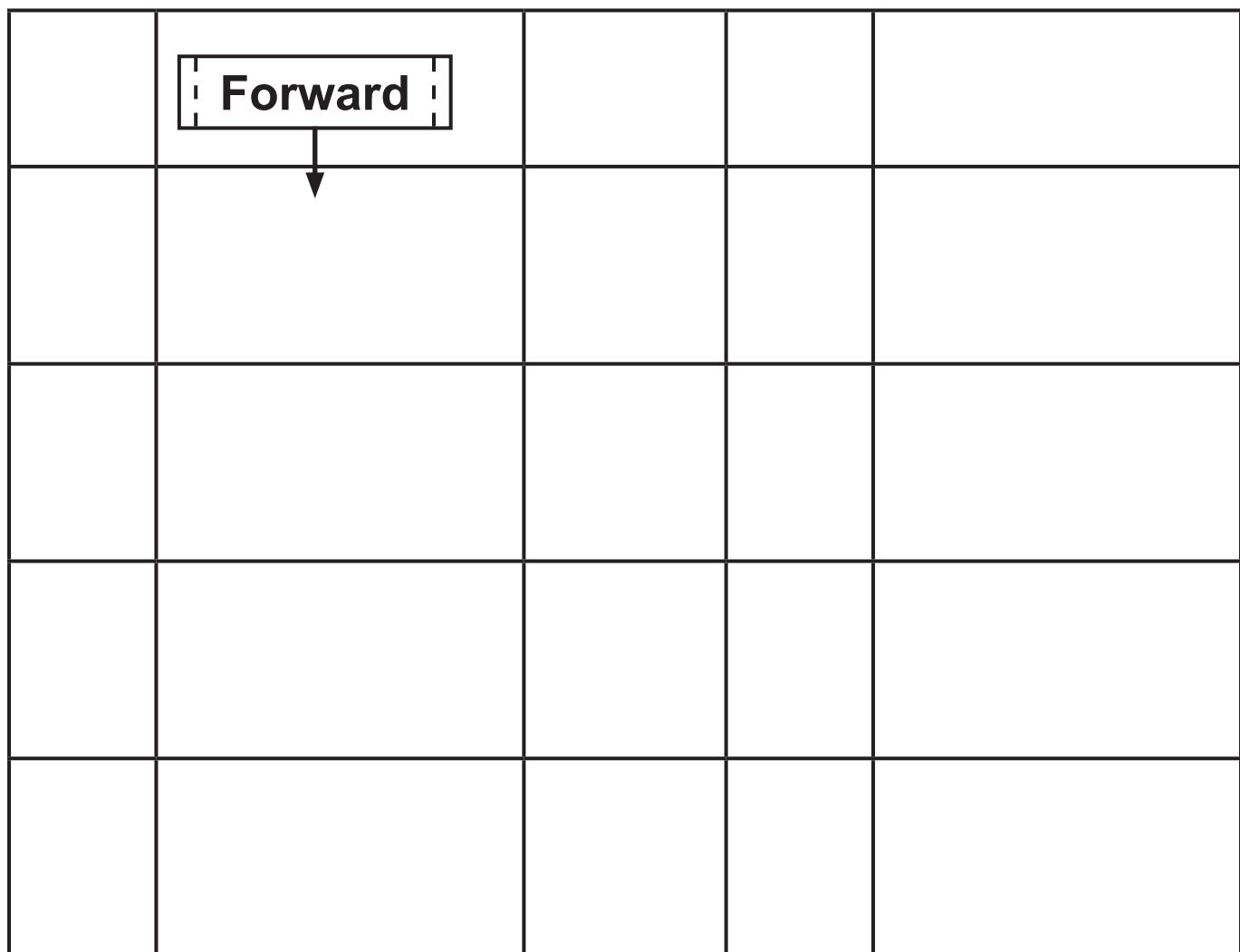

**Fig. 10**

(ii) Complete the flow chart in **Fig. 11** to represent the **Warning** macro as follows: [9 marks]


The buzzer with LEDs **1** and **2** will come on for one second and then switch off for one second. This sequence should operate **four** times before ending.



**Fig. 11**

(iii) Complete the flow chart in **Fig. 12** to represent the **Reverse & Turn** macro as follows: [9 marks]


The **Warning** macro will operate. The two motors **A** and **B** will turn on for four seconds, reversing the buggy before stopping. Motor **A** will switch on after a one second delay to turn the buggy to the right through  $90^\circ$ . This motor operates for three seconds, before switching off to end the macro.

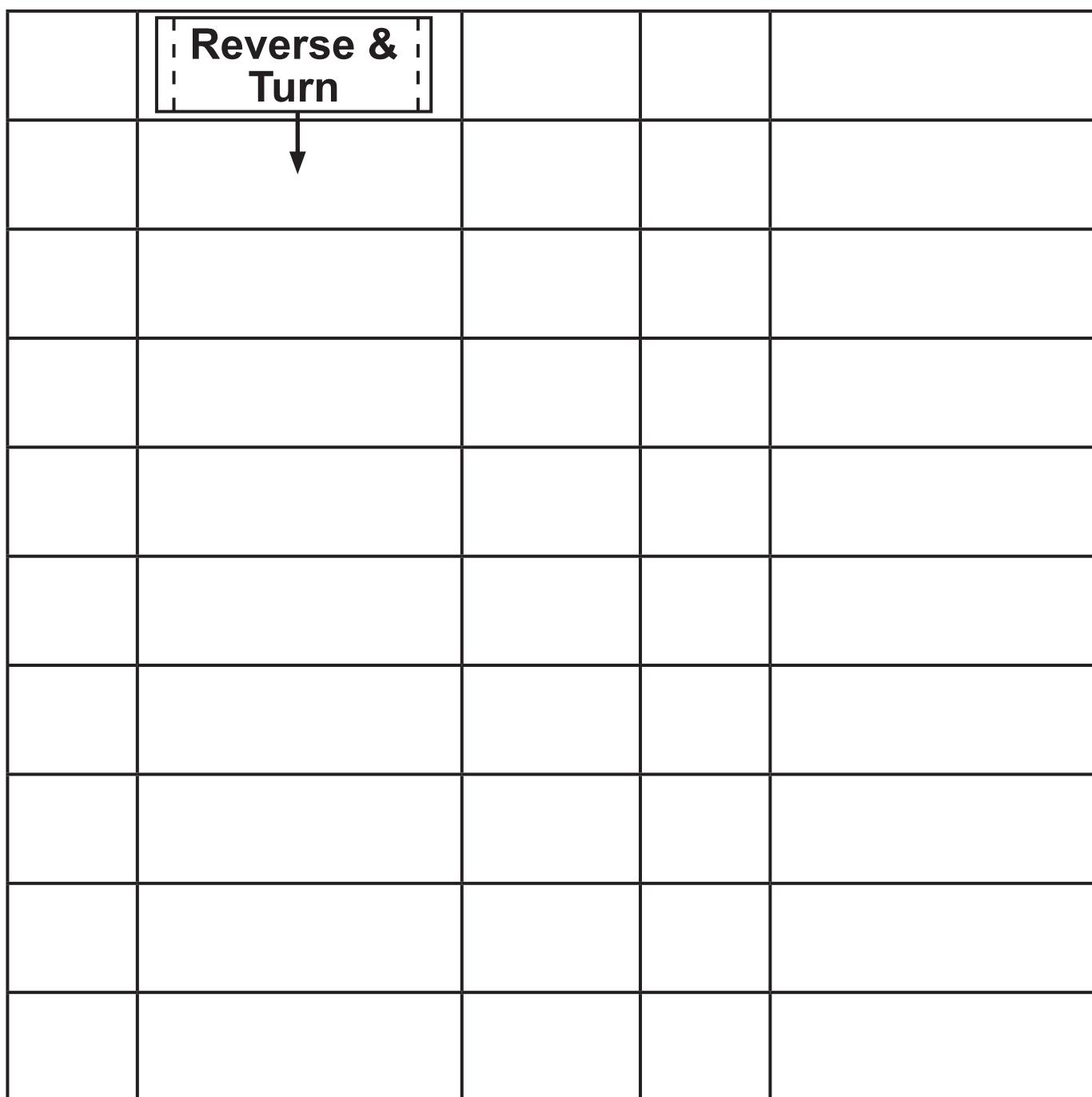

**Fig. 12**

(iv) Complete the flow chart in **Fig. 13** to show the full operation of the buggy. [10 marks]

When the slide switch is operated, the power LED is turned on and the **Forward** and **Reverse & Turn** macros will operate. There is then a two second delay. This process will repeat until the slide switch is turned off.

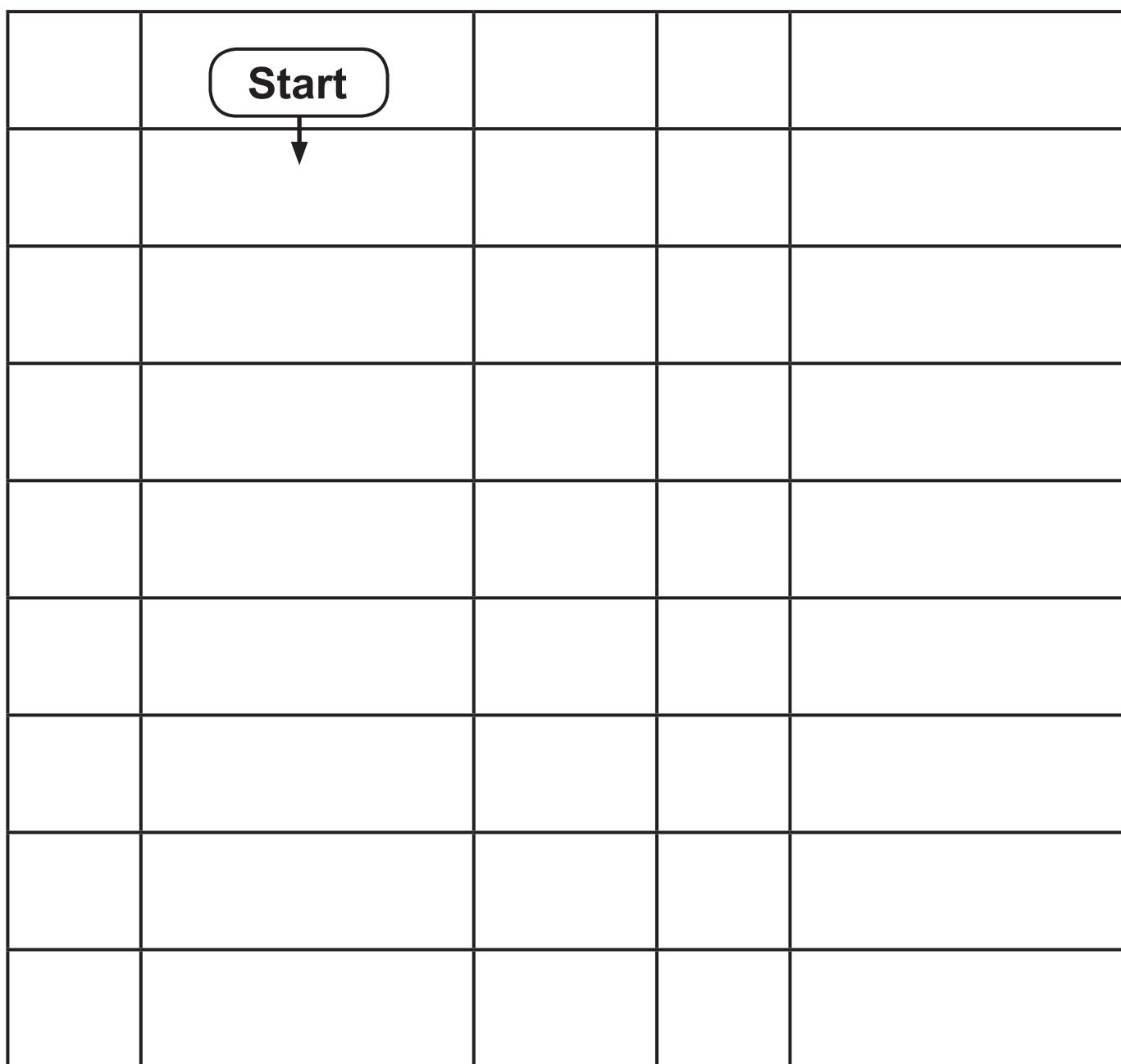

**Fig. 13**

---

**THIS IS THE END OF THE QUESTION PAPER**

---

For Examiner's use only	
Question Number	Marks
1	
2	
Total Marks	
Examiner Number	

Permission to reproduce all copyright material has been applied for.  
In some cases, efforts to contact copyright holders may have been unsuccessful and CCEA  
will be happy to rectify any omissions of acknowledgement in future if notified.