



Rewarding Learning

General Certificate of Secondary Education
2014

Centre Number

--	--	--	--	--

Candidate Number

--	--	--	--

Technology and Design

Unit 2:
Systems and Control

Element 1: Electronic and
Microelectronic Control Systems



[GTD21]

GTD21

TUESDAY 3 JUNE, AFTERNOON

TIME

1 hour.

INSTRUCTIONS TO CANDIDATES

Write your Centre Number and Candidate Number in the spaces provided at the top of this page.

Write your answers in the spaces provided in this question paper.

Questions which require drawing or sketching should be completed using an HB pencil. All other questions must be completed in blue or black ink only. **Do not write in pencil or gel pen.**

Answer **all** questions.

INFORMATION FOR CANDIDATES

The total mark for this paper is 80.

Figures in brackets printed down the right-hand side of pages indicate the marks awarded to each question or part question.

8687



20GTD2101



DO NOT WRITE ON THIS PAGE

8687



20GTD2102


Formulae for GCSE Technology and Design

You should use, where appropriate, the formulae given below when answering questions which include calculations.

1 Potential Difference = current \times resistance ($V = I \times R$)

2 For potential divider
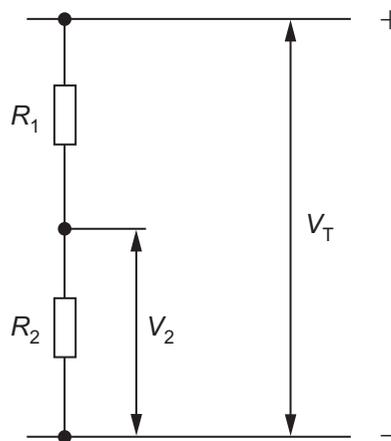
$$V_2 = \frac{R_2}{R_1 + R_2} \times V_T$$



3 Series Resistors $R_T = R_1 + R_2 + R_3 \text{ etc}$

Parallel Resistors $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$ or $R_T = \frac{R_1 \times R_2}{R_1 + R_2}$

4 Time Constant $T = R \times C$



Answer **all** questions.

- 1 (a) With reference to integrated circuits what does DIL mean? Explain with the aid of a sketch how pin one can be identified.

DIL _____ [1]

Sketch

Identity of pin one _____

_____ [2]

- (b) (i) Calculate the value of the single resistor which could replace the three resistors shown in **Fig. 1** below.

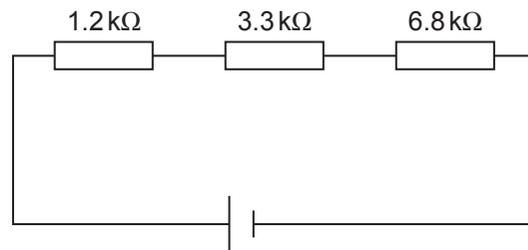


Fig. 1

Calculation

[2]





(ii) Using the colour code below identify the colour of the first three bands of the 6.8 kΩ resistor shown in Fig. 1.

0 = Black 1 = Brown 2 = Red 3 = Orange 4 = Yellow
 5 = Green 6 = Blue 7 = Violet 8 = Grey 9 = White

Colour of Band 1 _____

Colour of Band 2 _____

Colour of Band 3 _____ [3]

(iii) Calculate the combined value of the two resistors shown in Fig. 2 below. Each resistor has a value of 6.8 kΩ.

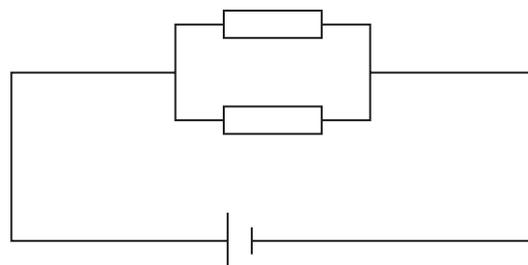


Fig. 2

Calculation

[3]

(iv) Calculate the maximum and minimum values that the 6.8 kΩ resistor may have if it has a 5% tolerance.

Calculation

[3]

[Turn over





2 The incomplete circuit diagram in **Fig. 6** shows part of a primary PIC circuit and a secondary circuit. The secondary circuit requires a 12 volt supply and a 12 volt motor.

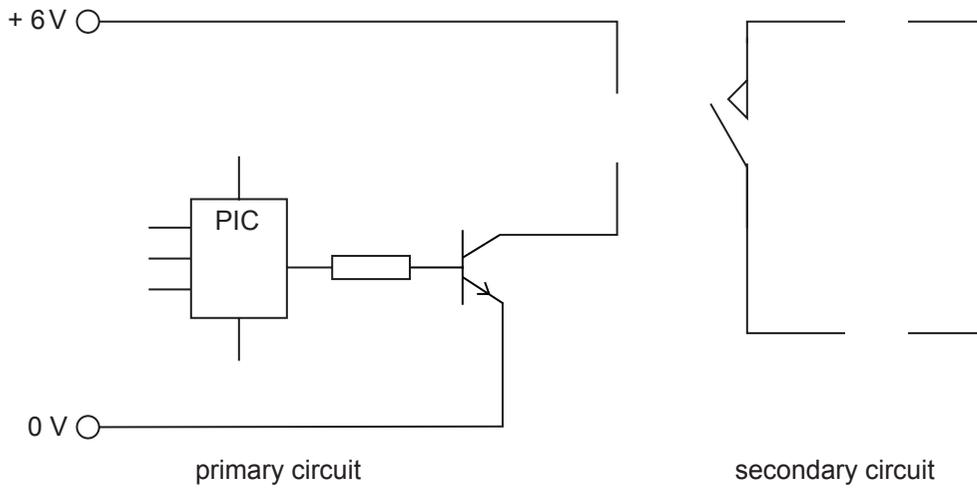


Fig. 6

Examiner Only	
Marks	Remark

(a) (i) Complete **Fig. 6** by inserting symbols for a relay coil, a diode, a 12 volt supply and a motor in the correct locations. [4]

(ii) What is the purpose of the diode in the circuit?

_____ [1]

(iii) Suggest a reason for the use of a secondary circuit.

_____ [1]



(b) An outline sketch of a steady hand game is shown in Fig. 7. The circuit to operate the steady hand game contains a PIC. The PIC flowchart includes 3 macros called, **DISPLAY**, **ATTEMPTS** and **SOUND**. Each macro will have a specific function:

- **DISPLAY** – to activate the 3 LEDs
- **ATTEMPTS** – to count the number of failed attempts
- **SOUND** – to activate a buzzer after the third failed attempt

To start the game the **DISPLAY** macro must first be turned on.

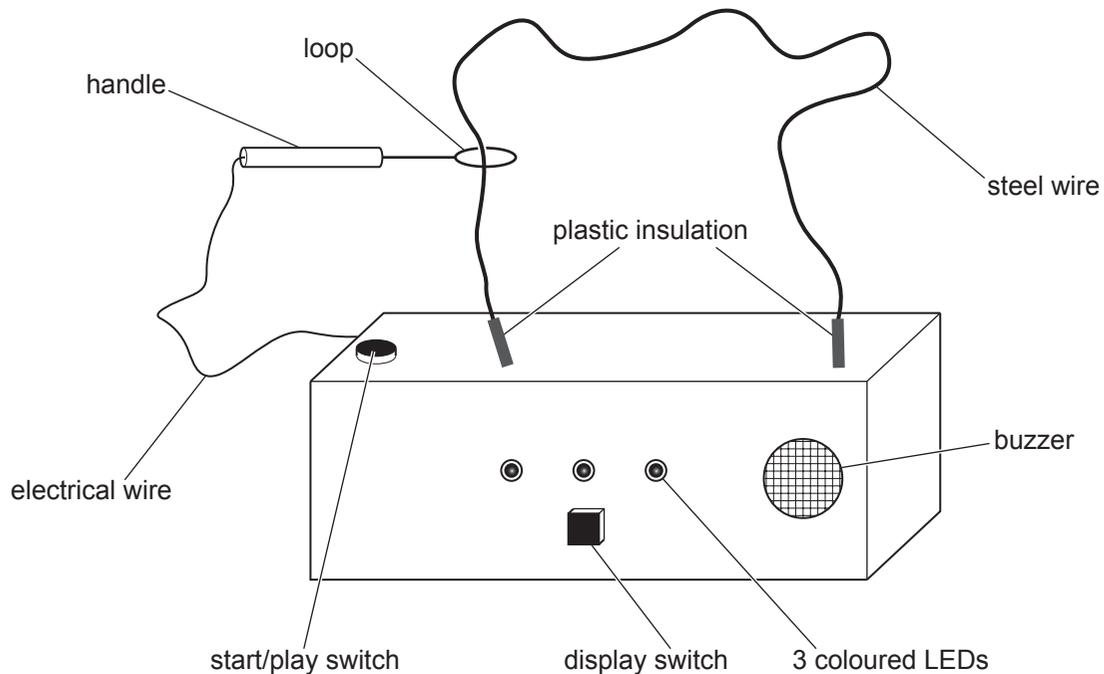


Fig. 7

Examiner Only

Marks Remark



Tables 1 and 2 show the inputs and outputs which are used in the PIC circuit.

Table 1

PIC Inputs	Not used	Not used	Start/Play Switch	Display Switch	Loop Contacts Steel Wire
BIT	4	3	2	1	0

Table 2

PIC Outputs	Not used	Not used	Not used	Buzzer	Not used	Green LED	Yellow LED	Red LED
BIT	7	6	5	4	3	2	1	0

Examiner Only	
Marks	Remark



(i) Macro 1 DISPLAY

A display showing 3 different coloured LEDs will operate when the display switch is turned on.

Complete the **DISPLAY** macro in **Fig. 8**. When the display switch is turned on a red LED will turn on. Then after 0.5 seconds a yellow LED will turn on and after another 0.5 seconds a green LED will turn on. When all the LEDs are on the macro ends.

Beside each input and output cell, indicate the relevant bit pattern.

DISPLAY		BIT PATTERN		
	↓			

Fig. 8

[10]

Examiner Only	
Marks	Remark



(iii) Macro 3 SOUND

When all the LEDs are turned off a buzzer will switch on and off five times.

Complete the **SOUND** macro in **Fig. 10** to enable the buzzer to switch on and off five times before ending. The buzzer should remain on for 2 seconds and switch off for 1 second each time.

Bit patterns are not required.

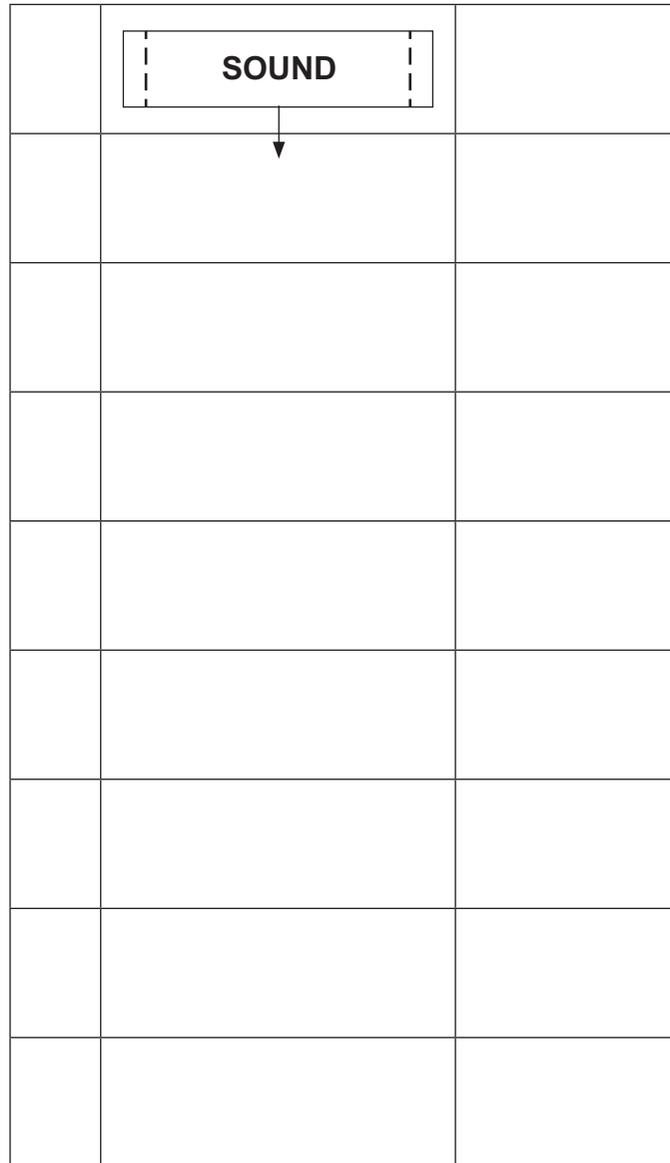


Fig. 10

[7]

Examiner Only	
Marks	Remark





THIS IS THE END OF THE QUESTION PAPER





DO NOT WRITE ON THIS PAGE

8687



20GTD2117

DO NOT WRITE ON THIS PAGE

8687



20GTD2118





DO NOT WRITE ON THIS PAGE

8687



20GTD2119

DO NOT WRITE ON THIS PAGE

For Examiner's use only	
Question Number	Marks
1	
2	

Total Marks	
--------------------	--

Examiner Number

Permission to reproduce all copyright material has been applied for. In some cases, efforts to contact copyright holders may have been unsuccessful and CCEA will be happy to rectify any omissions of acknowledgement in future if notified.

177996



20GTD2120

