

OCR

Oxford Cambridge and RSA

Wednesday 7 June 2017 – Afternoon**A2 GCE ELECTRONICS****F614/01** Electronic Control Systems

Candidates answer on the Question Paper.

OCR supplied materials:

None

Other materials required:

- Scientific calculator

Duration: 1 hour 40 minutes

Candidate forename		Candidate surname	
-----------------------	--	----------------------	--


Centre number						Candidate number				
---------------	--	--	--	--	--	------------------	--	--	--	--

INSTRUCTIONS TO CANDIDATES

- Write your name, centre number and candidate number in the boxes above. Please write clearly and in capital letters.
- Use black ink. HB pencil may be used for graphs and diagrams only.
- Answer **all** the questions.
- Read each question carefully. Make sure you know what you have to do before starting your answer.
- Write your answer to each question in the space provided. If additional space is required, you should use the lined page(s) at the end of this booklet. The question number(s) must be clearly shown.
- Do **not** write in the barcodes.

INFORMATION FOR CANDIDATES

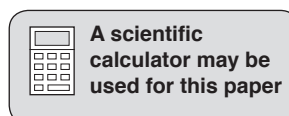- The number of marks is given in brackets [] at the end of each question or part question.
- The total number of marks for this paper is **110**.
- You will be awarded marks for your Quality of Written Communication.
- You are advised to show all the steps in any calculations.
- This document consists of **20** pages. Any blank pages are indicated.



Microcontroller instructions

The microcontroller contains eight general purpose registers S_n , where $n = 0, 1, 2 \dots 7$. The microcontroller has an eight bit input port, I, an eight bit output port, Q, and an analogue input, ADC.

In the table of assembler instructions given below, S_d is the destination register and S_s the source register.

assembler	function
MOVI S_d, n	Copy the byte n into register S_d
MOV S_d, S_s	Copy the byte from S_s to S_d
ADD S_d, S_s	Add the byte in S_s to the byte in S_d and store the result in S_d
SUB S_d, S_s	Subtract the byte in S_s from the byte in S_d and store the result in S_d
AND S_d, S_s	Logical AND the byte in S_s with the byte in S_d and store the result in S_d
EOR S_d, S_s	Logical EOR the byte in S_s with the byte in S_d and store the result in S_d
INC S_d	Add 1 to S_d
DEC S_d	Subtract 1 from S_d
IN S_d, I	Copy the byte at the input port into S_d
OUT Q, S_s	Copy the byte in S_s to the output port
JP e	Jump to label e
JZ e	Jump to label e if the result of the last ADD, SUB, AND, EOR, INC, DEC, SHL or SHR was zero
JNZ e	Jump to label e if the result of the last ADD, SUB, AND, EOR, INC, DEC, SHL or SHR was not zero
RCALL s	Push the program counter onto the stack to store the return address and then jump to label s
RET	Pop the program counter from the stack to return to the place the subroutine was called from
SHL S_d	Shift the byte in S_d one bit left putting a 0 into the lsb
SHR S_d	Shift the byte in S_d one bit right putting a 0 into the msb

There are three subroutines provided:

- readtable – copies the byte in the lookup table pointed at by S_7 into S_0 . The lookup table is labelled table: When $S_7=0$ the first byte from the table is returned in S_0
- wait1ms – waits 1ms before returning
- readadc – returns a byte in S_0 proportional to the voltage at ADC

Datasheet

resistance	$R = \frac{V}{I}$	
power	$P = VI$	
series resistors	$R = R_1 + R_2$	
time constant	$\tau = RC$	
monostable pulse time	$T = 0.7RC$	
relaxation oscillator period	$T = 0.5RC$	
frequency	$f = \frac{1}{T}$	
voltage gain	$G = \frac{V_{out}}{V_{in}}$	
open-loop op-amp	$V_{out} = A(V_+ - V_-)$	
non-inverting amplifier gain	$G = 1 + \frac{R_f}{R_d}$	
inverting amplifier gain	$G = -\frac{R_f}{R_{in}}$	
summing amplifier	$-\frac{V_{out}}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} \dots$	
break frequency	$f_0 = \frac{1}{2\pi RC}$	
Boolean Algebra	$A.\bar{A} = 0$	$A + \bar{A} = 1$
		$A.(B + C) = A.B + A.C$
	$\overline{A.B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}.\bar{B}$
	$A + A.B = A$	$A.B. + \bar{A}.C = A.B + \bar{A}.C + B.C$
amplifier gain	$G = -g_m R_d$	
ramp generator	$\Delta V_{out} = -V_{in} \frac{\Delta t}{RC}$	

Answer **all** the questions.

1 Fig. 1.1 shows a MOSFET circuit.

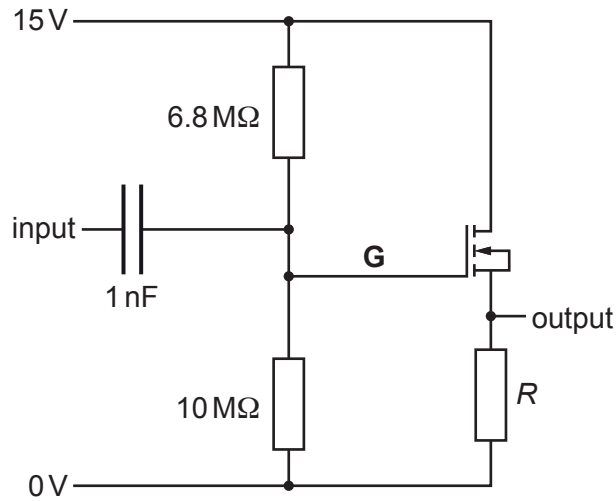


Fig. 1.1

(a) Show that the voltage at **G** is about 9V.

[2]

(b) Fig. 1.2 shows the behaviour of the MOSFET in Fig. 1.1.

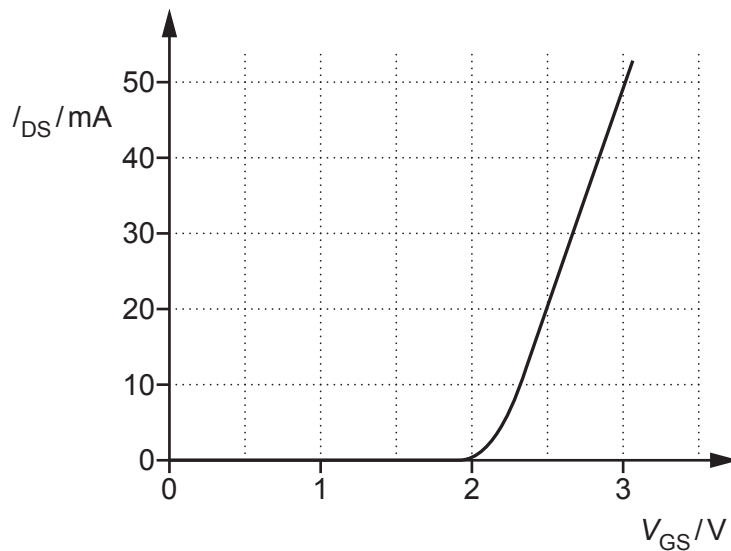


Fig. 1.2

(i) State the threshold voltage of the MOSFET in Fig. 1.1.

threshold voltage of MOSFET = V [1]

5

- (ii) When there is no signal at the input the current through R is 20 mA.
Calculate the voltage at the output when there is no signal at the input.

voltage at output = V [2]

- (iii) Calculate the value of the resistor R .

$R =$ Ω [1]

- (iv) Fig. 1.3 shows how the voltage at the input changes with time.
Draw on Fig. 1.3 to show how the voltage at the output changes with time.

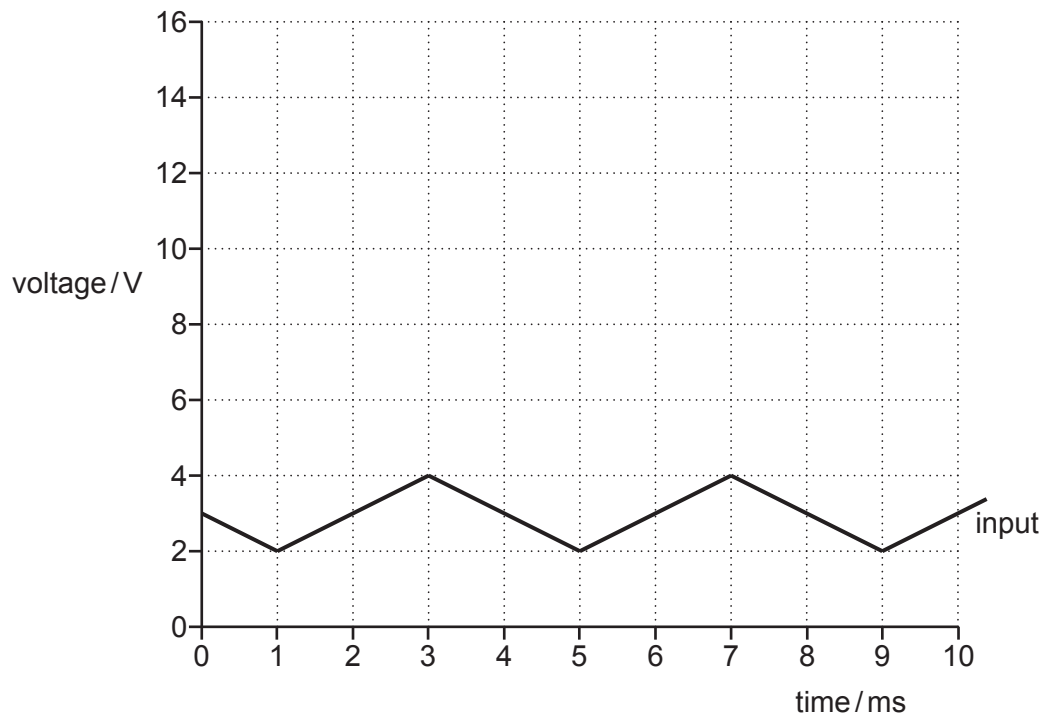


Fig. 1.3

[4]

- (c) Explain why the circuit in Fig. 1.1 is useful.

.....

 [2]

2 This question is about microcontrollers.

(a) State the function of the clock in a microcontroller.

.....
.....
..... [1]

(b) Explain the purpose of the reset pin on a microcontroller.
In your answer include the effect of activating the reset pin on any registers.

.....
.....
..... [2]

(c) Programs for microcontrollers are sometimes written in assembler.
Describe how programs written in assembler are converted to a form that the microcontroller can read.
State where programs are stored in the microcontroller.

.....
.....
.....
.....
.....
..... [3]

8

- 3 Fig. 3.1 shows the incomplete block diagram of a 4 x 4 bit *volatile* memory module.

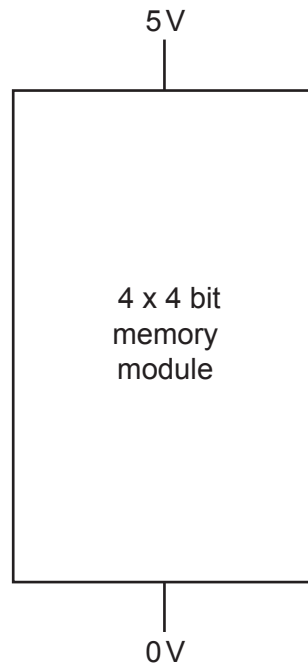


Fig. 3.1

- (a) State what is meant by *volatile* when referring to volatile memory.

.....
 [1]

- (b) Complete the block diagram of the 4 x 4 bit memory in Fig. 3.1 by adding labelled connections for each of the address lines, data lines and control lines.

[6]

- (c) The memory module is constructed from a number of memory cells. Calculate the number of memory cells in the memory module.

number of memory cells = [1]

(d) Draw a circuit diagram in the space below to show how a memory cell can be made from a D-type flip-flop and a tristate.

data ———

write ———

————— read

[5]

(e) Give **two** reasons why a tristate is needed in a memory cell.

.....

.....

.....

..... [2]

10

- 4 A MOSFET amplifier circuit is shown in Fig. 4.1.

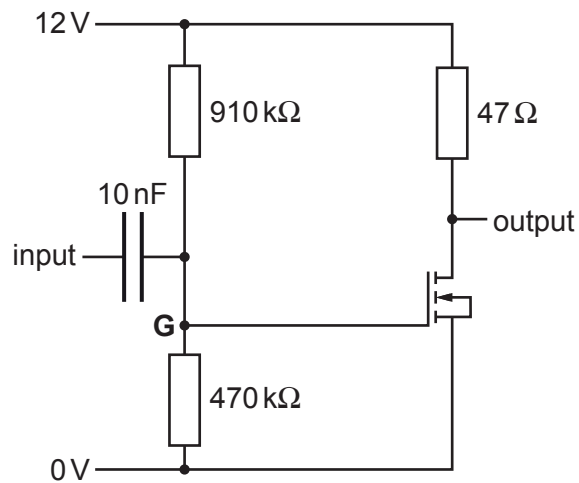


Fig. 4.1

- (a) Explain the purpose of the two resistors 910 kΩ and 470 kΩ in the amplifier circuit.

.....

.....

.....

.....

..... [3]

- (b) The graphs in Fig. 4.2 show how the output voltage depends on the signal at the input. Explain how these graphs show that the a.c. gain of the amplifier is about -7 .

.....

.....

.....

..... [3]

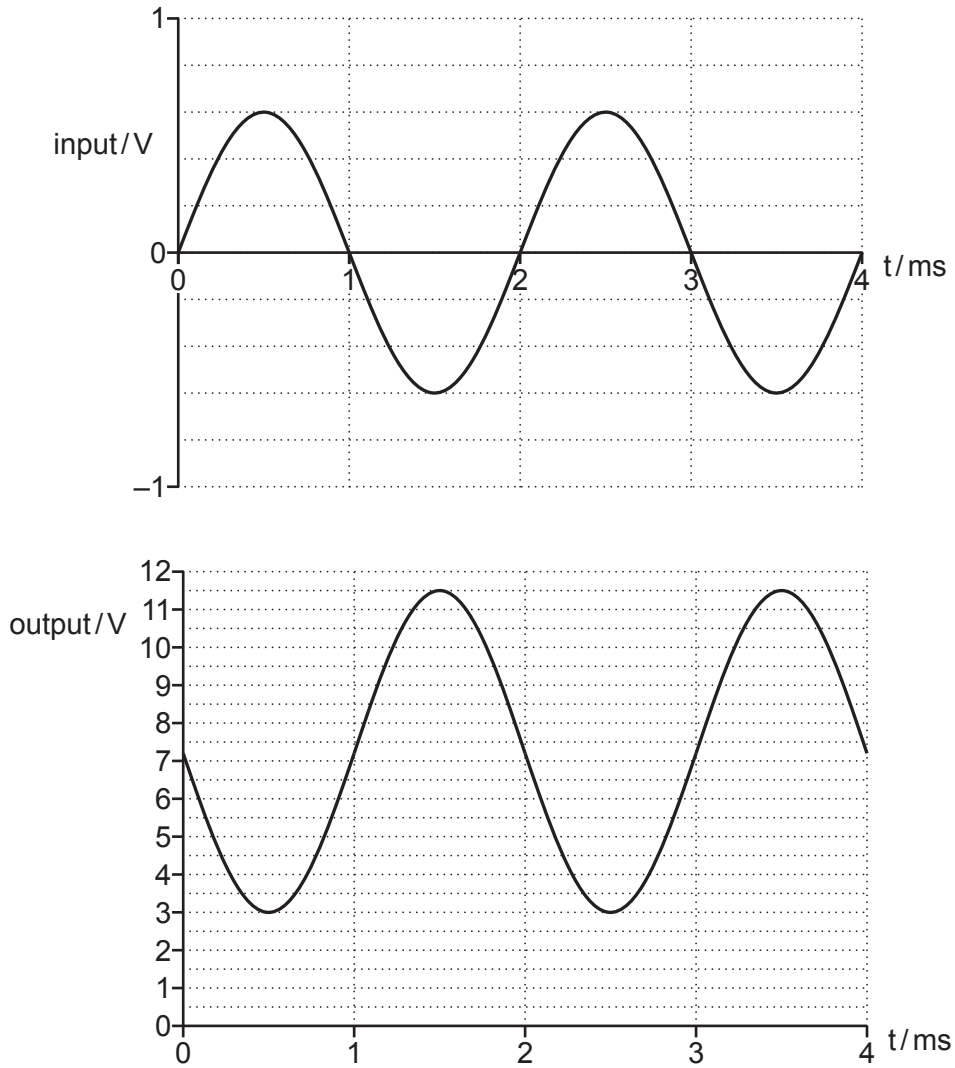


Fig. 4.2

(c) Calculate the transconductance of the MOSFET in Fig. 4.1.

transconductance = S [3]

(d) Calculate the threshold voltage of the MOSFET in Fig. 4.1.

threshold voltage = V [4]

5 This question is about a system that automatically keeps the temperature in a biology experiment constant.

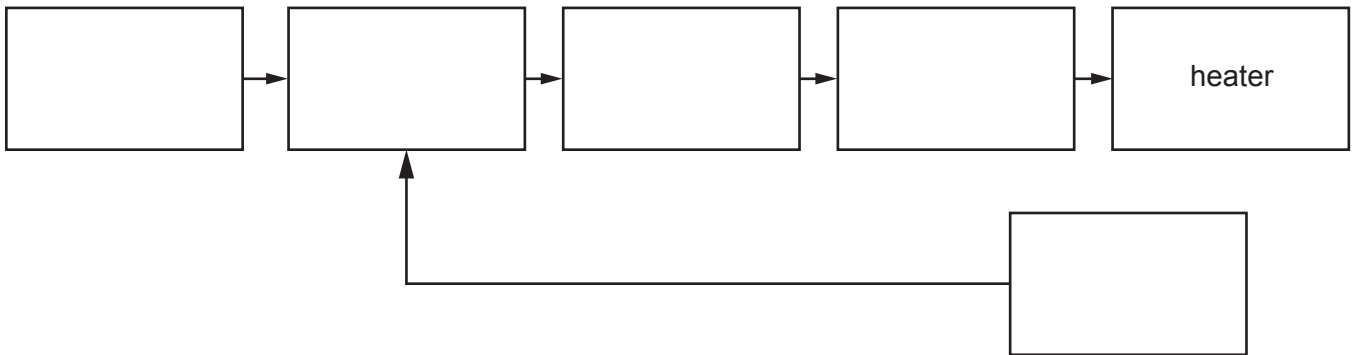


Fig. 5.1

(a) Use some of the terms below to complete the block diagram in Fig. 5.1 of a proportional control system for temperature.

- | | | | |
|-----------------------|-----------------------------|---------------------------|------------------------|
| AND gate | difference amplifier | opto-isolator | power amplifier |
| ramp generator | reference | temperature sensor | tristate |

[5]

(b) Draw the circuit diagram of a ramp generator in Fig. 5.2 below. Label the component values to make the output V_{out} change at -1 V/ms when the input voltage V_{in} is 2 V .

Justify your component values with a calculation.





Fig. 5.2

[6]

13

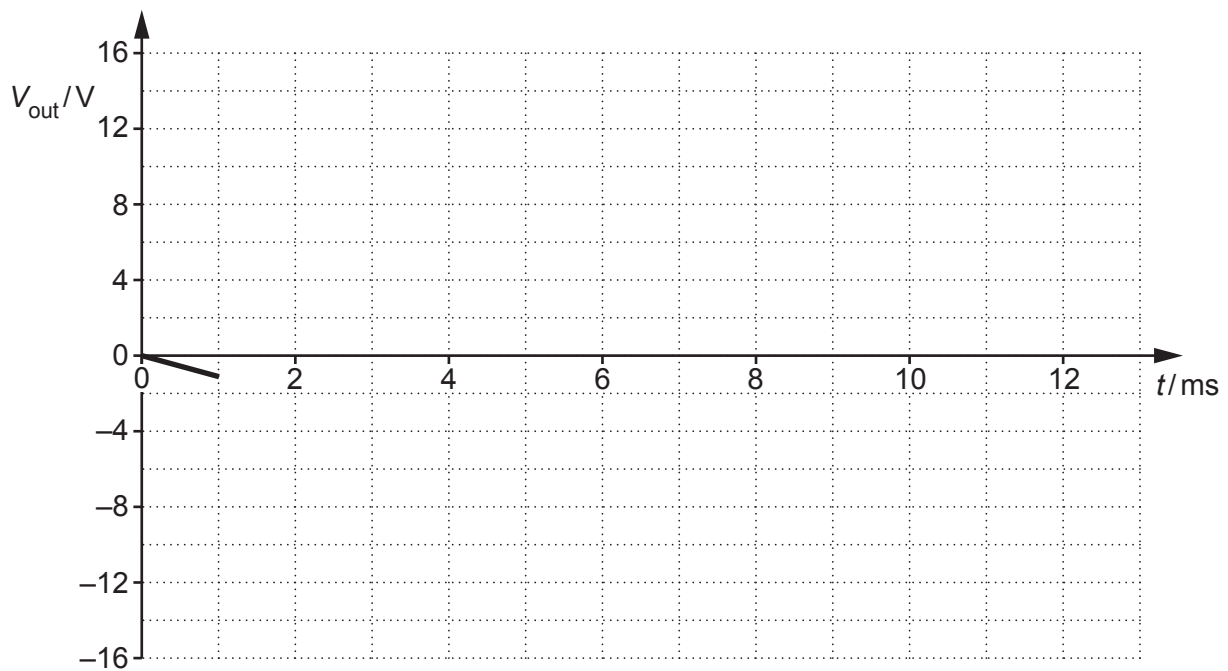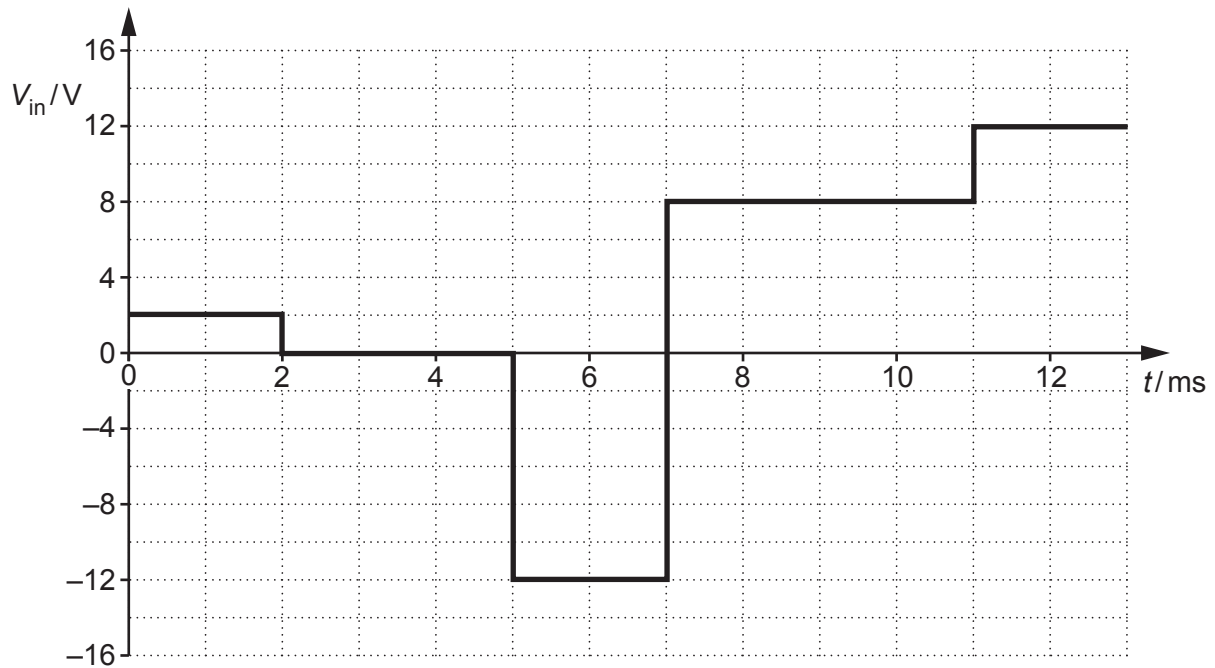- (c) The graph below shows how the input voltage V_{in} of the ramp generator in Fig. 5.2 varies with time.

Complete the graph to show how the output voltage V_{out} varies with time. V_{out} starts at 0V.



[6]

- 6 Fig. 6.1 shows the circuit and part of the program for scales used in a sweet factory to help the operator fill a bag with the correct weight of sweets.

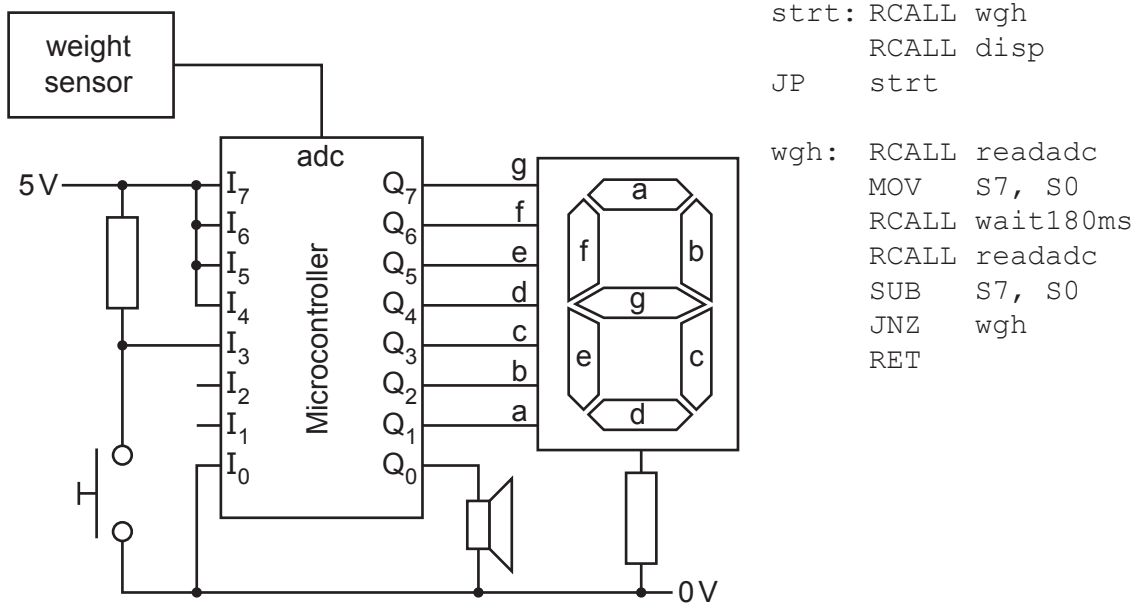


Fig. 6.1

- (a) Write the subroutine `wait180ms` to wait for 180ms before returning. You should use the subroutine `wait1ms` which waits for 1 millisecond in your subroutine.

```

wait180ms: .....
.....
.....
.....
.....
    
```

[5]

- (b) The subroutine `low` displays **L** on the display and the subroutine `high` displays **H** on the display in Fig. 6.1. The subroutines do not operate the speaker. Write the subroutines `low` and `high`.

```

low: .....
.....
.....

high: .....
.....
    
```

[4]

(c) Describe the effect of the subroutine `corr` on the output devices in Fig. 6.1.

```
corr: MOVI  S2, 01
      MOVI  S3, 40
      MOVI  S4, 90
bck:  OUT   Q, S4
      RCALL wait1ms
      RCALL wait1ms
      EOR   S4, S2
      DEC  S3
      JNZ  bck
      RET
```

.....

.....

.....

.....

.....

..... [4]

(d) Explain how the contents of the register affect what the subroutine `disp` does to the output devices in Fig. 6.1.

```
disp: MOVI  S5, 80
      AND   S5, S0
      JNZ  nxt1
      RCALL low
      JP   end
nxt1: MOVI  S5, 7C
      AND   S5, S0
      JNZ  nxt2
      RCALL corr
      JP   end
nxt2: RCALL high
end:  RET
```

.....

.....

.....

.....

.....

.....

.....

.....

.....

..... [5]

7 Fig. 7.1 shows the block diagram of a switched-mode power supply.

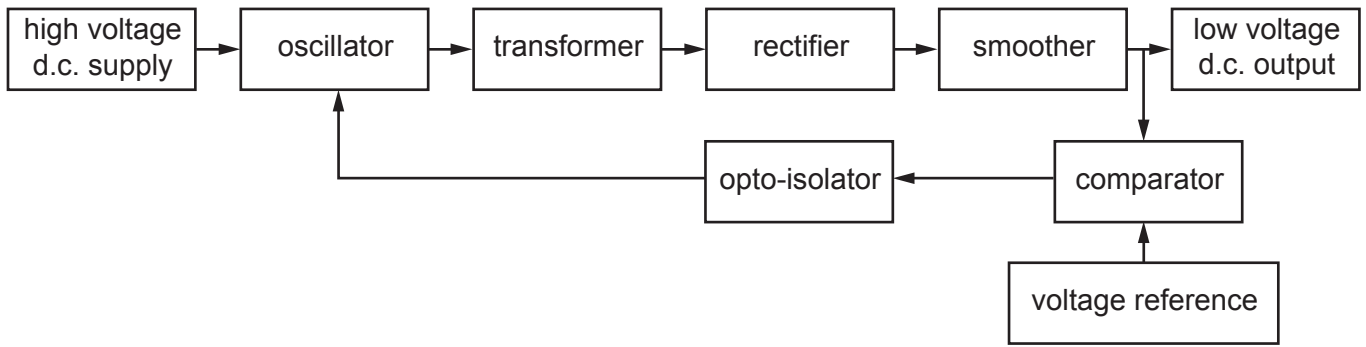


Fig. 7.1

(a) Explain why the oscillator is needed in the system in Fig. 7.1.

.....
 [1]

(b) Draw the circuit for a rectifier by adding four diodes and any necessary connections to Fig. 7.2.



Fig. 7.2

[2]

(c) Explain why the output voltage of a switched-mode power supply does not change when the high voltage input is reduced from 230 V to 110 V.

.....

 [3]

(d) State **two** other advantages of a switched-mode power supply over a power supply using just a transformer, rectifier, smoother and regulator.

.....

.....

.....

..... [2]

18

8 Fig. 8.1 shows a 4-bit register.

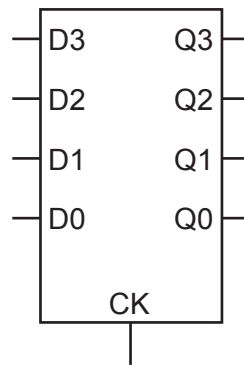


Fig. 8.1

- (a) Show how the 4-bit register can be constructed from D-type flip-flops. Label all of your connections.

[4]

- (b) Write the decimal number 37 in 7-bit binary in the boxes below.

--	--	--	--	--	--	--

[1]

19

- (c) A system for adding two binary numbers together using a full adder is shown in Fig. 8.2. Complete the diagram by filling in the empty boxes.

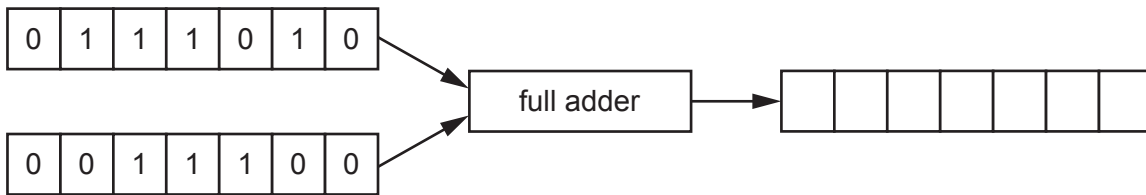


Fig. 8.2

[2]

- (d) Two's complement is used in digital systems to represent negative numbers. Show how you would represent the number -73 using two's complement.

Explain your working by first representing 73 as a binary number and then showing each step with a comment.

[4]

- (e) Complete the block diagram in Fig. 8.3 of a system for subtracting one number from another below. Use a full adder and a two's complement processor in your design.



Fig. 8.3

[2]

Quality of written response [3]

END OF QUESTION PAPER

ADDITIONAL ANSWER SPACE

If additional space is required, you should use the following lined page(s). The question number(s) must be clearly shown in the margin(s).

A large rectangular area with a solid vertical line on the left side and horizontal dotted lines across the rest of the page, providing space for writing answers.



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.