



GCE

Electronics

Unit **F615**: Communications Systems

Advanced GCE

Mark Scheme for June 2018

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, Cambridge Nationals, Cambridge Technicals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.










This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.

© OCR 2018


Annotations



1		31	BOD	Benefit of doubt
2		21	Cross	Cross
3		241	ECF	Error carried forward
4		191	NBOD	Benefit of doubt not given
5		1841	Not Relevant	Expandable vertical wavy line
6		271	REP	Repeat
7		201	TV	Too vague
8		11	Tick	Tick
9		1741	ZERO	Zero (big)

Question			Answer	Mark	Guidance
1	(a)	i	Red, green and blue (intensity) line (sync) frame (sync)	1 1 1	Not accept R,G,B, without words accept descriptions of function instead of name list principle applies to more than five responses
1	(a)	ii	any of the following for [1] each <ul style="list-style-type: none"> • noise/interference (picked up in transmission) • can be removed at video screen / receiver • using limiters / Schmitt triggers to restore signal • to improve picture quality • allows compression • for faster transmission • and/or less memory for storage • allows encoding/encryption • allows video / sound / text etc. • easier to store (in memory) • easier to edit picture • allows (time-division) multiplexing • allows for error detection/correction 	4	not faster unqualified
1	(b)	i	$2^7 = 128$	1	
1	(b)	ii	pixels per frame = $720 \times 1280 = 921600$; bits per frame = $921600 \times 7 = 6451200$;	1 1	ecf from incorrect pixels per frame
1	(b)	iii	20 Hz to 50 Hz image seen to flickers if frame rate too low (owtte)	1 1	
1	(b)	iv	bit rate = $6451200 \times 60 = 3.87 \times 10^8$; bandwidth = $0.5 \times 3.87 \times 10^8 = 193.5$ MHz (or about 200 MHz)	1 1	accept 102 / 100 MHz for [1] ecf incorrect calculated bit rate for [1] accept incorrect values for frame rate and/or bits per frame from b(ii) and b(iii) for [2] Correct answer = full marks.



Question	Answer	Mark	Guidance
----------	--------	------	----------

1	(c)	i	reduces bits (per frame / second); smaller bandwidth / less memory required;	1 1	accept faster transmission
1	(c)	ii	loss of quality / data	1	accept increased time delay / cost more because of extra circuitry

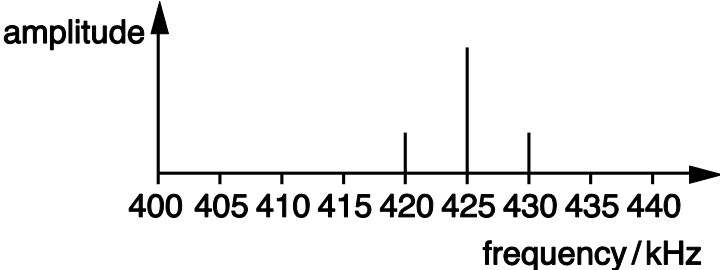Question			Answer	Mark	Guidance
2	(a)	i	amplitude of (carrier) at S determined by voltage of signal at M	1 1	
2	(a)	ii	spike at 425 kHz smaller same-height spikes at 420 kHz and 430 kHz 	2	
2	(b)		9.28 kΩ (accept 9.2 or 9.3) EITHER $I = (15 - 1.8) / 68 \times 10^3 = 1.94 \times 10^{-4} \text{ A}$ $R = 1.8 / 1.94 \times 10^{-4} = 9278$... OR $(15 - 2.2) / 2.2 = 47k/R_2$... OR $2.2 = 15 \times \frac{R_2}{47 + R_2}$	2	correct answer for [2] otherwise look for correct method for [1]
2	(c)		op-amp set up as amplifier for S; gain depends on resistance of MOSFET; which is determined by voltage at gate; so gain of amplifier altered by M;	1 1 1 1	

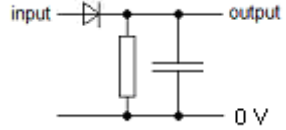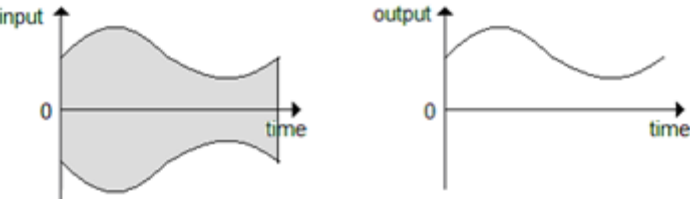Question			Answer	Mark	Guidance
2	(d)	i	<p>correct symbols for resistor, capacitor, diode circuit as shown below</p> 	1 1	Diode symbol doesn't need a line thro it.
2	(d)	ii	<p>diode rectifies signal / removes negative part of signal RC network filters out high frequency components sketch of AM signal at input sketch of matching demodulated signal at output</p> 	1 1 1 1	<p>accept smoothes signal</p> <p>accept output signal centred on zero</p>

Question		Answer	Mark	Guidance
3	(a)	Removes frequencies above audible Effectively removes the carrier wave	1 1	NOT remove unwanted / preserve wanted signals Accept correct operation of circuit as explanation for [2]
3	(b)		4	Correct NAND gate monostable with NOT gate at output [1] R at least 10kΩ [1] RC = 4μs (actually 4.3 μs) Use of T = 0.7 RC to justify values [1]
3	(c)	i	(108 - 87.5)/0.2 = 102.5 or 102	1 accept reverse calculation: 100 stations gives 205 kHz answer must be an integer
3	(c)	ii	FM bandwidth is 5f _s , AM bandwidth is 2f _s = 80 kHz channels = (108 - 87.5)/0.08 = 256 (or 250-60)	1 1 answer must be an integer ecf incorrect AM bandwidth between 10 and 100 kHz
3	(c)	iii	noise added to signal in transmission can be removed from FM by Schmitt trigger / limiter but not possible for AM	1 1 1 1 accept alternative answer: • AM codes with amplitude [1] • FM codes with frequency [1] • noise affect amplitude more than frequency [1]

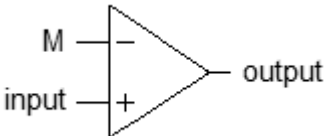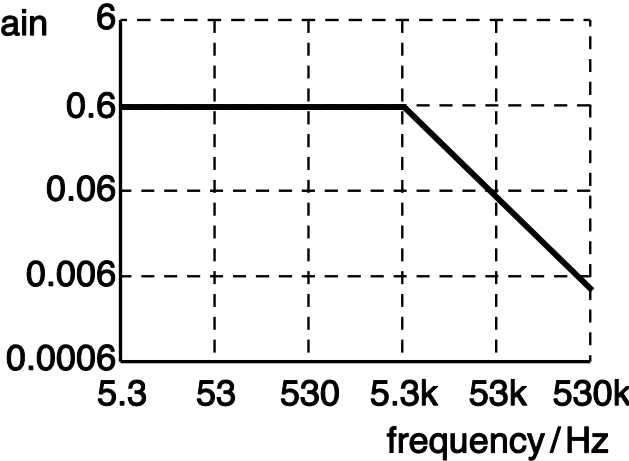Question		Answer	Mark	Guidance	
4	(a)	<p>ST threshold calculation</p> <ul style="list-style-type: none"> $I = 13/380k = 3.4 \times 10^{-5} \text{ A};$ $V = 3.4 \times 10^{-5} \times 150k = 5.13 \text{ V};$ <p>RG calculation</p> <ul style="list-style-type: none"> $\frac{4 \times 5.13}{T} = \frac{13}{56k \times 1.0n}$ $T = 8.8 \times 10^{-5} \text{ s}, \text{ so } f = 11.3 \text{ kHz};$ 	1 1 1 1	Method shown [1] Correct value [1] Method shown [1] Correct value [1] accept anything that rounds to 11 kHz with correct method for [2]	
4	(b)	i		2	comparator with any input to M [1] correct input and output labels [1]
4	(b)	ii	voltage at input; sets mark-space ratio of output;	1 1	ignore amplitude / signal ignore frequency ignore description of op-amp behaviour
4	(c)	i	<p>gain</p>  <p>frequency/Hz</p>	5	$= - \frac{R_f}{R_{in}}$ <p>use of R_{in} to calculate low frequency gain of (-) 0.6 [1]</p> $f_0 = \frac{1}{2\pi RC}$ <p>use of $2\pi RC$ to calculate break frequency of 5.3 kHz [1] suitable log axes labelled [1] correct shape [1] correct break frequency [1]</p> <p>accept 5.3, 53, 530 ... as frequency axis labels</p>

Question			Answer	Mark	Guidance
4	(c)	ii	break frequency is close to maximum signal frequency that can be correctly coded; need at least two samples per signal cycle; maximum signal frequency should be $11.3 / 2 = 5.65$ kHz;	1 1 1	

Question		Answer	Mark	Guidance
5	(a)	noise is random signal (from components) interference is signal from other electrical systems	1 1	
5	(b)	any three of the following, [1] each single cable: <ul style="list-style-type: none"> • picks up interference from other electrical systems; • introduces random signal (noise); both cables in twisted-pair: <ul style="list-style-type: none"> • pick up same interference; • have different noise; • have opposite (polarity) of signal; difference amplifier <ul style="list-style-type: none"> • rejects interference; • transmits signal (and noise) 	3	
5	(c)		2	each correct link for [1] reject multiple links

Question			Answer	Mark	Guidance
6	(a)	i	$X_L = 2\pi \times 1.6 \times 10^{-3} \times 40 \times 10^3;$ $= \underline{402} \Omega;$	2	substitution [1] evaluation for [1]
6	(a)	ii		2	straight line through 400 Ω , 40 kHz [1] gradient of 45 degrees [1] accept missing label
6	(a)	iii		1	

Question			Answer	Mark	Guidance
6	(b)	i	$f_0^2 = \frac{1}{4\pi^2 LC}$ <p>e.g. specify 1.6 mH = L</p> <p>so $C = \frac{1}{4\pi^2 f_0^2 L}$</p> $= \frac{1}{4\pi^2 \times (390 \times 103)^2 \times 1.6 \text{ mH}}$ $= 104 \text{ pF}$	1 1 1 1	use of formula specify a value for either L or C powers of 10 answer
6	(b)	ii	to create sharper filter than simple LC circuit; so that only one carrier + sidebands gets through;	1 1	accept labelled gain-frequency graphs accept to improve selectivity

Question		Answer	Mark	Guidance
7	(a)	- 0.2;	1	
7	(b)	A at +5 V; E at -0.5; resolution = $-0.5 \times -0.2 = 0.1$ V;	1 1 1	ecf from 7(a) ecf: A = 1 V gives 0.05 V for [2]
7	(c)	CBA = 111 and use of summing amplifier formula; top of range is 0.7 V; bottom of range is 0 V;	1 1 1	

Question			Answer	Mark	Guidance
8	(a)	i		2	each bit correct for [1] stop bit must be immediately after D
8	(a)	ii	start bit tells receiver that word is about to arrive; stop bit returns cable to resting state (wtte);	1 1	not tells receiver that word is complete
8	(b)	i	maximum bit rate = $2 \times 12 = 24$ Mbits per second; so each bit lasts for $1/24 \times 10^6 = 42$ ns	1 1	accept reverse calculation not 128 ns
8	(b)	ii	each packet lasts for $1024 \times 42 \times 10^{-9} = 43 \mu\text{s}$; so packets per second = $1 / 43 \mu\text{s} = 23000 \text{ s}^{-1}$	1 1	ignore $10 \mu\text{s}$ delay between packets accept 16×10^3 or 15×10^3 allow ecf from incorrect packet length

Question		Answer	Mark	Guidance																														
9	(a)	$V = 5 - 2.1 = 2.9 \text{ V};$ $R = 2.9/5 \times 10^{-3} = 580\Omega;$	1 1																															
9	(b)	i	2																															
		$B \cdot \overline{W.X} + \overline{X.Y}$ for [2] $B \cdot (\overline{W.X}).(\overline{X.Y})$ for [1]																																
9	(b)	ii	4	[1] per correct column ecf on incorrect W, X, Y: $B \cdot \overline{W.X.Y} \cdot \overline{W.X.Y}$ no ecf from (b)(i)																														
		<table border="1"> <thead> <tr> <th>Input signal</th> <th>W</th> <th>X</th> <th>Y</th> <th>B</th> <th>A</th> </tr> </thead> <tbody> <tr> <td>0.25 V</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0.75 V</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1.55 V</td> <td>0</td> <td>1</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>2.65 V</td> <td>1</td> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table>	Input signal	W	X	Y	B	A	0.25 V	0	0	0	1	1	0.75 V	0	0	1	0	0	1.55 V	0	1	1	1	0	2.65 V	1	1	1	0	1		
Input signal	W	X	Y	B	A																													
0.25 V	0	0	0	1	1																													
0.75 V	0	0	1	0	0																													
1.55 V	0	1	1	1	0																													
2.65 V	1	1	1	0	1																													
9	(c)	number of levels = $(2^{\text{word length}}) = 2^2 = 4$ resolution = range/number of levels = $2.8/4 = 0.7 \text{ V}$	1 1	accept words, codes for levels accept reverse argument look for explanation and calculation for each mark																														
9	(d)	time for on cycle = $2 \times 12 \times 10^{-6} = 24 \times 10^{-6} \text{ s};$ frequency = 42 kHz / 42000Hz;	1 1	83000 Hz = 1 mark																														

OCR (Oxford Cambridge and RSA Examinations)
The Triangle Building
Shaftesbury Road
Cambridge
CB2 8EA

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2018

 **Cambridge
Assessment**

