

**OCR**

Oxford Cambridge and RSA

**Monday 6 June 2016 – Afternoon****LEVEL 1/2 CAMBRIDGE NATIONAL IN SYSTEMS CONTROL IN  
ENGINEERING****R113/01** Electronic principles

Candidates answer on the Question Paper.

**OCR supplied materials:**

None

**Other materials required:**

- A calculator may be used

**Duration:** 1 hour

Candidate forename		Candidate surname	
-----------------------	--	----------------------	--

Centre number						Candidate number				
---------------	--	--	--	--	--	------------------	--	--	--	--

**INSTRUCTIONS TO CANDIDATES**

- Use black ink. HB pencil may be used for graphs and diagrams only.
- Complete the boxes above with your name, centre number and candidate number.
- Answer **all** the questions.
- Write your answer to each question in the space provided. Additional paper may be used if necessary but you must clearly show your candidate number, centre number and question number(s).
- Do **not** write in the bar codes.

**INFORMATION FOR CANDIDATES**

- The total number of marks for this paper is **60**.
- The number of marks for each question is given in brackets [ ] at the end of the question or part question.
- Dimensions are in millimetres unless stated otherwise.
- Quality of written communication will be assessed in questions marked with an asterisk (\*).
- This document consists of **12** pages. Any blank pages are indicated.



**A calculator may  
be used for this  
paper**


Answer **all** the questions.

1 (a) Complete the table by naming each component from its symbol.

Symbol	Component

[4]

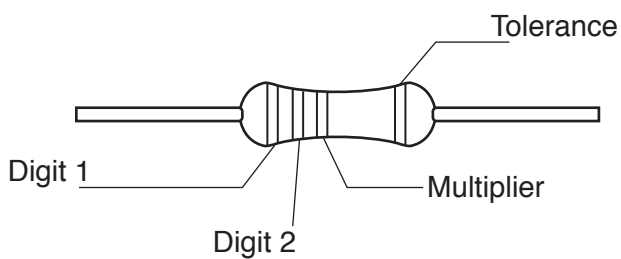(b) Fig. 1 shows a fixed resistor and a resistor colour code chart.



Digit 1	Digit 2	Multiplier	Tolerance
black 0	black 0	black 0	brown 0.01
brown 1	brown 1	brown 1	red 0.02
red 2	red 2	red 2	gold 0.05
orange 3	orange 3	orange 3	
yellow 4	yellow 4	yellow 4	
green 5	green 5	green 5	
blue 6	blue 6	blue 6	
violet 7	violet 7	gold 0.1	
grey 8	grey 8	silver 0.01	
white 9	white 9		

Fig. 1

Use the resistor colour code chart to determine the band colours of a resistor of value  $24\text{ k}\Omega \pm 5\%$ .

Digit 1 .....

Digit 2 .....

Multiplier .....

Tolerance .....

[2]

3

- (c) Determine the total resistance of three resistors, with values of  $10\ \Omega$ ,  $6.8\ \Omega$  and  $8.2\ \Omega$ , that are connected in series.

.....  
..... [1]

- (d) Fig. 2 shows a potential divider circuit.

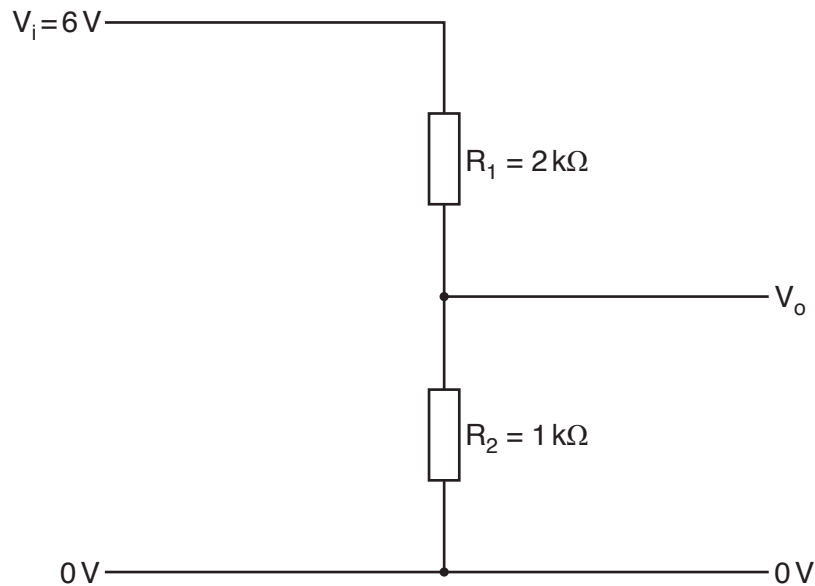


Fig. 2

Calculate the output voltage  $V_o$ .

.....  
.....  
.....  
..... [3]



3 Fig. 4 shows an operational amplifier (op amp).

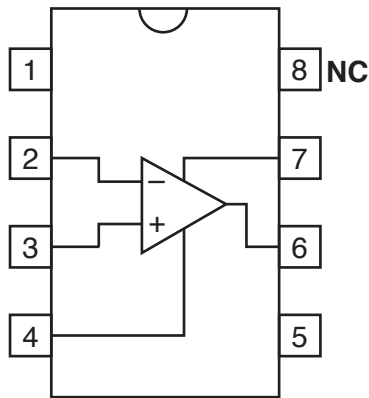


Fig. 4

(a) On Fig. 4, label the terminals 2, 3, 4, 6 and 7 with the following terms:

- Supply  $+V_{cc}$
- Supply  $-V_{cc}$
- Output
- Non-inverting input
- Inverting input.

[5]

(b) State what is meant by **NC** on terminal 8.

..... [1]

(c) Describe with the aid of a labelled diagram, the use of the operational amplifier as a comparator.

.....

.....

.....


.....

.....


.....

..... [5]

4 Fig. 5 shows **two** types of switch.

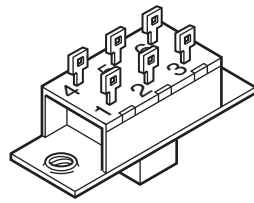

Switch A

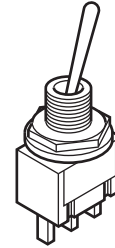

Switch B

Fig. 5

(a) From the list below name each type of switch.

- Double Pole Single Throw
- Double Pole Double Throw
- Micro
- Toggle

Switch A .....

Switch B .....

[2]

(b) Draw the graphical symbol of a reed switch.

[1]

(c) State which **two** of the following are output devices:

- Buzzer
- Microphone
- Solenoid
- Photodiode.

1 .....

2 .....

[2]



5 (a) Explain what is meant by the term 'portable appliance testing' (PAT).

.....  
..... [2]

(b) Name **three** PAT tests that are carried out on a portable electrical appliance.

1 .....

2 .....

3 ..... [3]

(c) Fig. 7 shows a 13A plug with its cover removed.

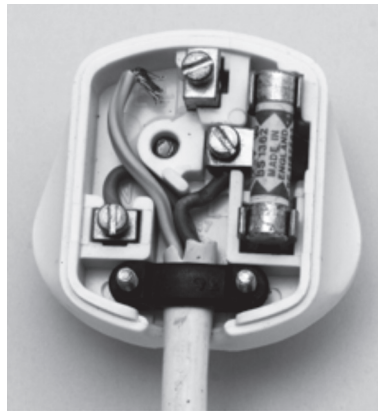


Fig. 7

Explain why this plug should not be connected to an electrical supply.

.....  
.....  
..... [2]



- (d) A label is attached to an appliance to show it has passed a portable appliance test (PAT). One item of information included on the label is the date of the test.

Name **two** other pieces of information that would be included on the label.

1 .....

2 .....

[2]



11

.....

.....

..... [6]

**END OF QUESTION PAPER**

**PLEASE DO NOT WRITE ON THIS PAGE**



**Copyright Information**

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website ([www.ocr.org.uk](http://www.ocr.org.uk)) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.