

**OCR**

Oxford Cambridge and RSA

# Level 3 Cambridge Technical in Engineering

## 05822/05823/05824/05825

### Unit 4: Principles of electrical and electronic engineering

## Tuesday 24 May 2016 – Afternoon

### Time allowed: 1 hour 30 minutes

**You must have:**

- the formula booklet for Level 3 Cambridge Technical in Engineering (inserted)
- a ruler (cm/mm)
- a scientific calculator

<b>First Name</b>						<b>Last Name</b>					
<b>Centre Number</b>						<b>Candidate Number</b>					
<b>Date of Birth</b>											

**INSTRUCTIONS**

- Use black ink. You may use an HB pencil for graphs and diagrams.
- Complete the boxes above with your name, centre number, candidate number and date of birth.
- Answer **all** the questions.
- Write your answer to each question in the space provided. If additional space is required, you should use the lined page(s) at the end of this booklet. The question number(s) must be clearly shown.

**INFORMATION**

- The total mark for this paper is **60**.
- The marks for each question are shown in brackets [ ].
- Where appropriate, your answers should be supported with working. Marks may be given for a correct method even if the answer is incorrect.
- An answer may receive no marks unless you show sufficient detail of the working to indicate that a correct method is being used.
- Final answers should be given to a degree of accuracy appropriate to the context.
- This document consists of **16** pages. Any blank pages are indicated.

FOR EXAMINER USE ONLY	
Question No	Mark
1	/10
2	/10
3	/11
4	/10
5	/8
6	/11
<b>Total</b>	<b>/60</b>

Answer **all** questions.

**1 (a)** An electrical fan is rated at 300 W and is connected to a 240 V mains supply for five hours.


**(i)** Calculate the energy used by the fan.

.....  
 ..... [2]

**(ii)** Calculate the current drawn by the fan motor.

.....  
 ..... [2]

**(b)** Fig. 1 shows a resistor network.

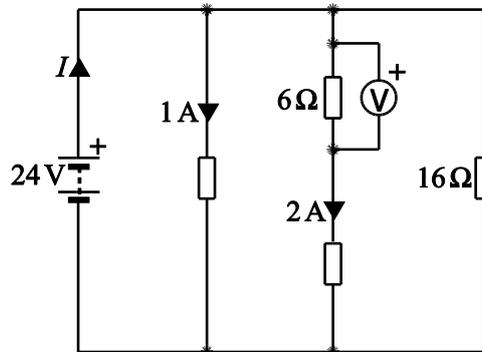

**Fig. 1**

**(i)** Calculate the value that will be displayed on the voltmeter.

.....  
 ..... [2]

(ii) Calculate the current  $I$ .

.....

.....

.....

..... [4]

2 (a) Draw a phasor diagram to represent a purely inductive AC circuit.

[2]

(b) A capacitor of  $22 \mu\text{F}$  is connected in series with a  $50 \Omega$  resistor across a supply of frequency  $60 \text{ Hz}$ .

Calculate the impedance ( $Z$ ).

.....

.....

.....

..... [4]

(c) Calculate the phase angle for the circuit shown in Fig. 2.

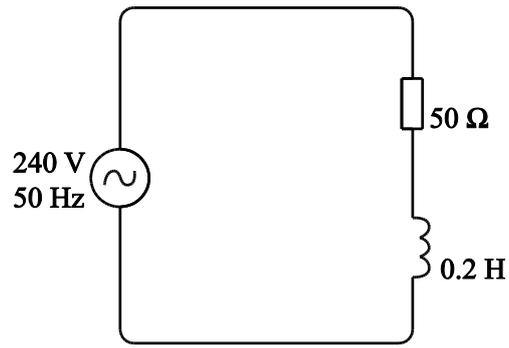


Fig. 2

.....

.....

.....

..... [4]

3 (a) State the function of a simple generator.

.....  
..... [1]

(b) Explain with the aid of labelled diagrams the difference between a series-wound DC motor and a shunt-wound DC motor.

.....  
.....  
..... [4]

(c) A 240 V shunt wound DC motor draws a current of 30 A. The motor has a field winding resistance of  $100\ \Omega$  and the armature resistance  $0.4\ \Omega$ .

(i) Calculate the current in the field winding.

.....  
..... [2]

(ii) Calculate the e.m.f. ( $E$ ) that occurs in the DC motor.

.....  
.....  
.....  
..... [4]

4 (a) Explain with the aid of labelled diagrams how a power supply **or** electrical components can be protected by:

(i) the use of a fuse.

.....  
..... [2]

(ii) the use of a diode.

.....  
..... [2]

- (b) An AC voltage is input into a full wave rectifier. Sketch the output voltage of the rectifier on labelled axes.

[2]

- (c) Explain with the aid of a labelled diagram how full wave rectification of an AC waveform can be achieved by using two diodes.

.....

.....

.....

..... [4]

5 (a) Describe the difference between a digital signal and an analogue signal.

.....

..... [2]

(b) Fig. 3 shows an electronic circuit used as a preamplifier in a domestic audio system.

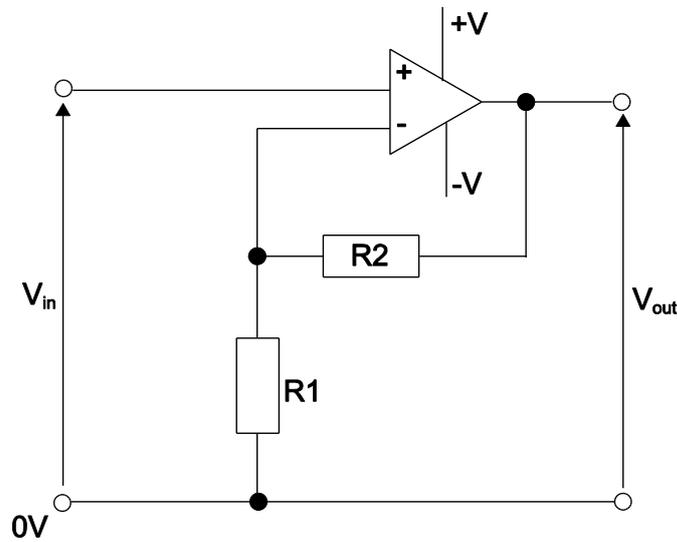


Fig. 3

(i) State the name of the circuit and explain the function of the resistors in this circuit.

Name of circuit.....

.....

.....

.....

..... [3]

(ii) The voltage gain for the circuit in Fig. 3 is given by:

$$\text{Voltage Gain} = 1 + \frac{R_2}{R_1}$$

If  $R_1 = 10 \text{ K}\Omega$ ,  $R_2 = 100 \text{ K}\Omega$  and the input voltage is  $0.2 \text{ V}$ , calculate the output voltage of the circuit.

.....

.....

..... [3]

6 (a) Complete the table below by drawing the circuit symbol for each of the logic gates identified.

Logic Gate Name	Circuit Symbol
NAND	
XOR	

[2]

(b) Fig. 4 shows part of a combinational logic circuit used in an engine management system.

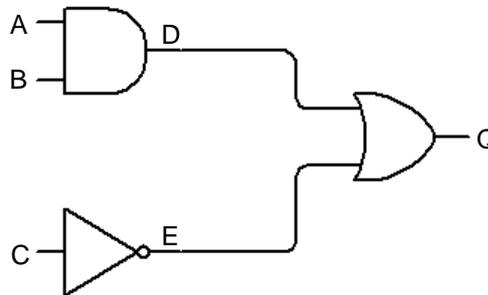


Fig. 4

Complete the truth table for this logic circuit, giving the logic levels at A, B, C, D, E and Q.

A	B	C	D	E	Q

[4]

(c) Draw the combinational logic circuit represented by the Boolean expression

$$Q = \overline{(A + B)}.C.$$

[2]

(d) Explain with the aid of a circuit symbol the function of a T-type bistable.

.....

.....

..... [3]

**END OF QUESTION PAPER**

**ADDITIONAL ANSWER SPACE**

If additional space is required, you should use the following lined page(s). The question number(s) must be clearly shown.

This section contains a large area of lined paper for writing answers. It features a vertical solid line on the left side, creating a margin. The rest of the page is filled with horizontal dotted lines, providing a guide for writing. The lines are evenly spaced and extend across the width of the page.

A vertical solid line is positioned on the left side of the page. From this line, 25 horizontal dotted lines extend across the page, creating a series of rows for writing. The dotted lines are evenly spaced and cover most of the page's height.

A large rectangular area with a solid vertical line on the left side and horizontal dotted lines extending across the page, providing a grid for writing answers.



Oxford Cambridge and RSA

**Copyright Information:**

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website ([www.ocr.org.uk](http://www.ocr.org.uk)) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.