



Cambridge Technicals

Engineering

Unit 4: Principles of electrical and electronic engineering

Level 3 Cambridge Technical Certificate/Diploma in Engineering

05822 - 05825

Mark Scheme for June 2018

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, Cambridge Nationals, Cambridge Technicals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.


All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.


Mark schemes should be read in conjunction with the published question papers and the report on the examination.


© OCR 2018


Annotations

<i>Annotation</i>	<i>Meaning</i>
tick	Correct response
cross	Incorrect response
Omission mark (carat)	Incomplete response
ECF	Error carried forward
BOD	Benefit of doubt
NBOD	No benefit of doubt
RE	Rounding error









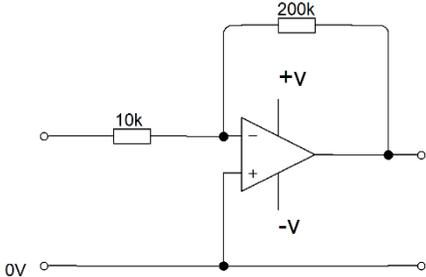
Question			Answer	Marks	Guidance
1	(a)	(i)	<p>Select R_{input} – Any suitable value between $1K\Omega$ and $100K\Omega$. For example: If $R_{input} = 10 (K\Omega)$ $R_{feedback} = -A_v R_{input}$ $= - (-20 \times 10K\Omega)$ $R_{feedback} = 200 (K\Omega)$</p>	<p>1</p> <p>1</p> <p>1</p> <p>1</p>	<p>Note: $R_{feedback}$ could be selected and R_{input} calculated.</p> <p>Rearrangement</p> <p>Substitution</p> <p>Do not accept negative values of R</p>
		(ii)	 <p>Correct op amp symbol Correct position of R_{input} Correct position of $R_{feedback}$ Connection of non-inverting input to 0V Values correctly added.</p>	<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p>	<p>Condone omission of power supply</p> <p>Allow ECF from 1(a)(i)</p>

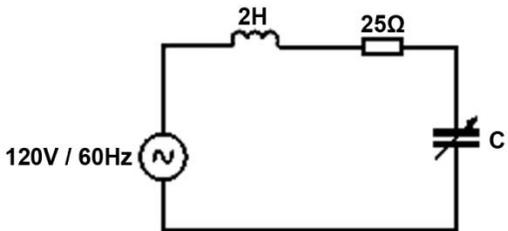Question			Answer	Marks	Guidance
2	(a)	(i)	 <p>Variable capacitor Resistor with value, Inductor with value, Supply with value, All components connected in series</p>	<p>1 1 1 1 1</p>	<p>Allow any sensible and unambiguous symbol for C_{var} Unit not required for the mark Unit not required for the mark Unit not required for the mark</p>
		(ii)	$2\pi fL = \frac{1}{2\pi fC}$ $2 \cdot \pi \cdot 60 \cdot 2 = \frac{1}{2 \cdot \pi \cdot 60 \cdot C}$ $(2 \cdot \pi \cdot 60 \cdot 2)^2 \cdot 2 = \frac{1}{C}$ $284245 = \frac{1}{C}$ <p>$C = 3.5 \mu\text{F}$ or 0.00000035 F or $3.5 \times 10^{-6} \text{ F}$</p>	<p>1 1 1 1 1</p>	<p>Correct formulae selection Substitution Rearrangement Correct answer Correct unit</p>

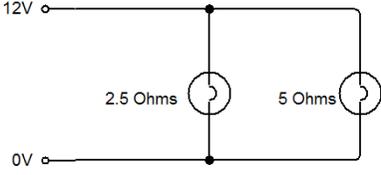Question			Answer	Marks	Guidance
3	(a)	(i)	 <p>2 lamps in parallel Supply in parallel Correct values</p>	1 1 1	Max 2 marks awarded if lamps are in series Award marks if units not stated.
		(ii)	$\frac{1}{R_{Total}} = \frac{1}{R_1} + \frac{1}{R_2}$ $\frac{1}{R_{Total}} = \frac{1}{2.5} + \frac{1}{5} = \frac{3}{5}$ $R_{Total} = 1.67 (\Omega)$	1 1 1	For applying knowledge from Unit 2 LO3 For applying knowledge from Unit 2 LO3 Substitution 1.7/1.67
		(iii)	$P = V^2/R$ $= 12^2/5$ $= 28.8\mathbf{W}$ <p>Or</p> $P = VI$ $I = 12/5 = 2.4A$ $P = 12 \times 2.4A = 28.8\mathbf{W}$	1 1 1 (1) (1) (1)	For applying knowledge from Unit 2 LO3 For applying knowledge from Unit 2 LO3 Allow ECF 29/28.8 For applying knowledge from Unit 2 LO3 For applying knowledge from Unit 2 LO3 Allow ECF 29/28.8
		(iv)	$W = PT$ $W = 28.8 \times 1.5$ $W = 43.2 \mathbf{Wh}$	1 1 1	For applying knowledge from Unit 2 LO3 For applying knowledge from Unit 2 LO3 Allow ECF Allow correct numerical answers in 0.043/0.0432 kWh / 160000 J / 155520 J / 160/156/155.5 KJ. <u>Not (k)Ws</u>

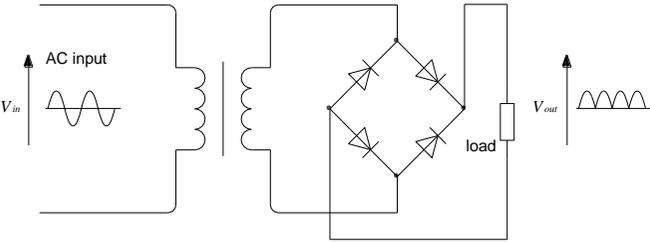Question			Answer	Marks	Guidance
4	(a)	(i)		<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p>	<p>Output voltage indicated correctly</p> <p>Input voltage indicated correctly</p> <p>2 diodes in bridge.</p> <p>2 diodes connected correctly</p> <p>4 Diodes connected correctly.</p>
		(ii)	<p>V_{in} – Sine wave</p>  <p>V_{out} – Fully rectified sine wave</p> 	<p>1</p> <p>1</p>	<p>At least one complete cycle must be seen</p> <p>At least one complete cycle must be seen</p>
	(b)		<p>$2\pi f = 126$</p> <p>$f = 126/2\pi = 20.1$ (Hz)</p>	<p>1</p> <p>1</p>	

Question		Answer	Marks	Guidance															
5	(a)	<table border="1"><thead><tr><th><i>A</i></th><th><i>B</i></th><th><i>Q</i></th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	<i>A</i>	<i>B</i>	<i>Q</i>	0	0	1	0	1	1	1	0	1	1	1	0	2	1 mark for every 2 correct rows
<i>A</i>	<i>B</i>	<i>Q</i>																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	

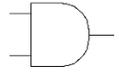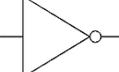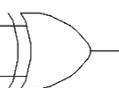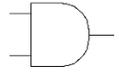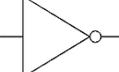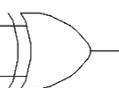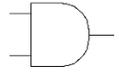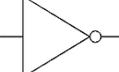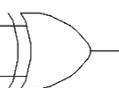Question		Answer	Marks	Guidance																									
(b)		<table border="1"> <thead> <tr> <th>Logic Gate</th> <th>Boolean Expression</th> </tr> </thead> <tbody> <tr> <td></td> <td>$Q = A.B$</td> </tr> <tr> <td></td> <td>$Q = \overline{A + B}$</td> </tr> <tr> <td></td> <td>$Q = \overline{A}$</td> </tr> <tr> <td></td> <td> or $Q = A \oplus B$ $\overline{A}.B + A.\overline{B}$ </td> </tr> </tbody> </table>	Logic Gate	Boolean Expression		$Q = A.B$		$Q = \overline{A + B}$		$Q = \overline{A}$		or $Q = A \oplus B$ $\overline{A}.B + A.\overline{B}$	1	The first logic gate expression has been completed in the question.															
		Logic Gate	Boolean Expression																										
			$Q = A.B$																										
			$Q = \overline{A + B}$																										
	$Q = \overline{A}$																												
	or $Q = A \oplus B$ $\overline{A}.B + A.\overline{B}$																												
1																													
1																													
1																													
(c)	(i)	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> <th>Y</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	X	Y	Q	0	0	1	0	0	0	1	0	0	1	1	0	0	0	1	1	1	0	1	0	6	1 mark for every 2 correct entries in the X column. 1 mark for every 2 correct entries in the Y column. 1 mark for every 2 correct entries in the Q column.
	A	B	X	Y	Q																								
0	0	1	0	0																									
0	1	0	0	1																									
1	0	0	0	1																									
1	1	0	1	0																									
	(ii)	Exclusive Or or XOR	1	Allow ECF (if relevant)																									

Question		Answer	Marks	Guidance
6	(a)	<p>Purpose of a motor starter:</p> <ul style="list-style-type: none"> To protect from overload or faults A Motor Starter is used for the smooth starting of a motor. It consists mainly of a variable resistance placed in series with the armature <p>The purpose of this resistance is:</p> <ul style="list-style-type: none"> To increase the resistance incrementally Thus restricting the armature current to a safe value To disconnect the motor in case of an overload To disconnect the motor when the field current is reduced beyond limit <p>Any four valid points (1 mark/point) stated.</p>	4	
	(b)	<p>Purpose and operation of a no volt coil:</p> <ul style="list-style-type: none"> To disconnect the motor if the supply voltage fails Provide automatic tripping when there is a major voltage dip Prevents the motor restarting when the power supply is switched on When the power supply is cut the coil demagnetises and the starter handle spring returns to the 'off' position. <p>Any four valid points (1 mark/point) used to explain purpose and operation of the no volt coil.</p>	4	

OCR (Oxford Cambridge and RSA Examinations)
The Triangle Building
Shaftesbury Road
Cambridge
CB2 8EA

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2018

 **Cambridge
Assessment**

