



Cambridge Technicals Engineering

Unit 4: Principles of electrical and electronic engineering

Level 3 Cambridge Technical Certificate/Diploma in Engineering
05822 - 05825

Mark Scheme for January 2019

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, Cambridge Nationals, Cambridge Technicals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.

© OCR 2019

Annotations


Annotation	Meaning
tick	Correct response
cross	Incorrect response
Omission mark (carat)	Incomplete response
ECF	Error carried forward
BOD	Benefit of doubt
NBOD	No benefit of doubt
Wtte	Words to that effect

Subject-specific marking instructions


In all numerical calculation questions a correct response will gain all marks unless specified otherwise.



Rounding of answers should be to the same number of significant figures as the data in the question, or, otherwise, an answer will be correct provided it rounds to the correct answer.







Symbols used in circuit diagrams must identify relevant components uniquely and unambiguously.

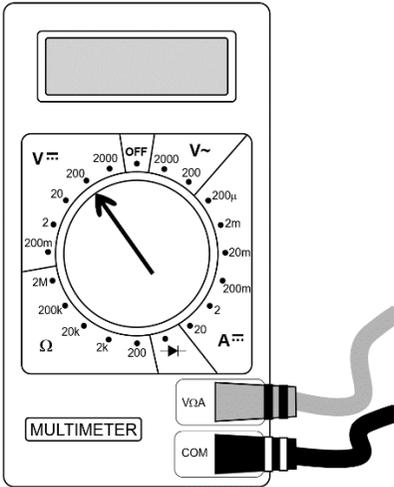
Question			Answer	Marks	Guidance
1	(a)	(i)	$20\ \Omega + 40\ \Omega = 60\ \Omega$	1	Unit given in question
1	(a)	(ii)	$I = \frac{V}{R} = \frac{9}{60} = 0.15\text{ A}$ Correct numerical answer (0.15) Correct units A	1 1	For applying knowledge from Unit 2 LO3 Accept A, mA or μA etc. 150 mA for [2]
1	(a)	(iii)	$V = IR = 0.15 \times 40 = 6\text{ V}$ ecf from (ii)	1	Unit given in question
1	(a)	(iv)	$P = IV = 0.15 \times 6 = 0.9\text{ W}$ ecf from (ii) and (iii)	1	Unit given in question
1	(b)	(i)	 <p style="text-align: center;">200 V DC</p>	1	
1	(b)	(ii)	maximum number of decimal places (1) e.g.: Setting on 200 provides <u>maximum number of decimal places</u> (wtte) for accuracy of measurement without going over range.	1	Mark for understanding 'maximum number of decimal places'


Question			Answer	Marks	Guidance
1	(c)	(i)	$6 - 1.8 = 4.2 \text{ V}$	1	
1	(c)	(ii)	0.8 mA	1	
1	(c)	(iii)	$0.8 - 0.6 = 0.2 \text{ mA}$	1	
1	(c)	(iv)	$R_1 = \frac{V_1}{I_1} = \frac{1.8}{0.0008} = 2250 \Omega$	1	2.25 k Ω Accept answer to 2sf: 2300 Ω Accept e.c.f. from 1(c)(ii) for I_1
1	(c)	(v)	$R_t = \frac{V}{I_2} = \frac{4.2}{0.0002} = 21000 \Omega$ $R_t = R_2 + 18000$ $\therefore R_2 = 21000 - 18000 = 3000 \Omega$	1	Full marks for any method that gives 3000 Ω or 3 k Ω Accept e.c.f. from 1(c)(iii) for I_2 and/or for V from 1(c)(i)
2	(a)	(i)	6 V	1	
2	(a)	(ii)	2 ms	1	
2	(a)	(iii)	12 V	1	Not $\pm 6 \text{ V}$
2	(a)	(iv)	$T = 2 \text{ ms} = 2 \times 10^{-3} \text{ s}$ $f = \frac{1}{T} = \frac{1}{2 \times 10^{-3}} = 500 \text{ Hz}$	1 1 1	<i>For applying knowledge from Unit 2 LO3</i> Conversion of ms to s or use of kHz in answer Use of $f=1/T$ to get answer ecf from conversion and 1(a)(ii) Correct units in answer (Hz or kHz)

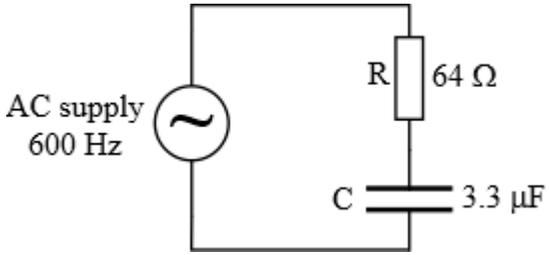
Question			Answer	Marks	Guidance
2	(b)	(i)	Correct symbols used for R and C. Series circuit of three elements with correct values	1 1	Accept US resistor symbol  Accept any symbols for this mark 
2	(b)	(ii)	$f = 600\text{Hz}$ $C = 3.3\mu\text{F} = 3.3 \times 10^{-6}\text{F}$ $X_C = \frac{1}{2\pi \times 600 \times 3.3 \times 10^{-6}} = 80\Omega$	1 1 1	<i>For applying knowledge from Unit 2 LO3</i> Conversion to F Successful calculation using correct values ecf from conversion to F Correct units
2	(b)	(iii)	$Z = \sqrt{R^2 + X_C^2} = \sqrt{64^2 + 80^2} = 102\Omega$ ecf from 2bii	1	Ignore units Accept answer to 2sf: 100Ω Accept answers 102.7 Ω or 103 Ω from using the precise answer to 2(b)ii of 80.38 Ω.

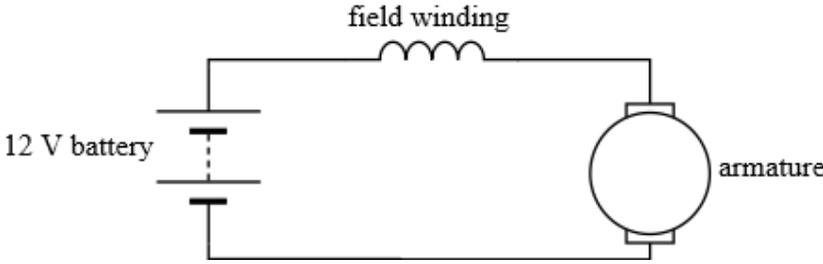
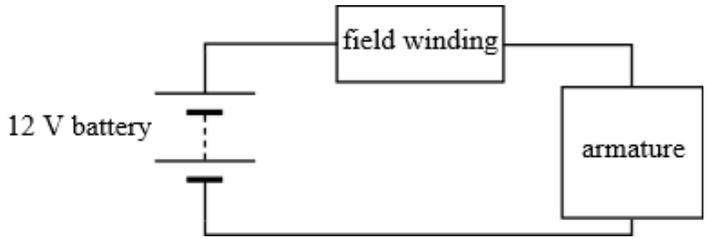
Question		Answer	Marks	Guidance
3	(a)	A series wound DC motor is used to start a car engine. When a voltage is first applied to the motor it is not turning and so the EMF generated by the motor is zero and the torque provided by the motor is high . After a short time the motor has reached high speed and so the EMF generated by the motor is high and the torque provided by the motor is low .	1 1 1 1	1 mark for each correct word: zero high high low
3	(b)		1	Accept any labelled symbols for field winding and armature in series with the battery. 
3	(c) (i)	$R_t = 0.20 \Omega$	1	
3	(c) (ii)	Selection of correct formula $V = E + I_a R_t$ seen or implied $E = V - I_a R_t = 12 - (20 \times 0.2) = 8(V)$ Mark for correct units = V	1 1 1	Allow ecf for R_t from 3(c)(i) Award mark for 8 regardless of units <i>For applying knowledge from Unit 2 LO3</i>

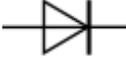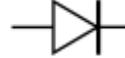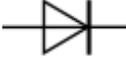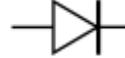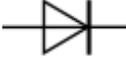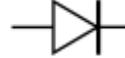Question	Answer	Marks	Guidance														
<p>4 (a)</p>	<p>1 mark for each correct link</p> <table border="0" style="width: 100%;"> <thead> <tr> <th style="text-align: left;">Block</th> <th style="text-align: left;">Function</th> </tr> </thead> <tbody> <tr> <td style="border: 1px solid black; padding: 2px;">rectifier</td> <td style="border: 1px solid black; padding: 2px;">produces a constant 5 V regardless of whether it is providing a large current for a flat phone battery or a small current to a fully charged phone</td> </tr> <tr> <td style="border: 1px solid black; padding: 2px;">smoothing circuit</td> <td style="border: 1px solid black; padding: 2px;">reduces the 230 V AC to a much lower AC voltage</td> </tr> <tr> <td style="border: 1px solid black; padding: 2px;">stabilising circuit (load regulator)</td> <td style="border: 1px solid black; padding: 2px;">converts alternating current to direct current</td> </tr> <tr> <td style="border: 1px solid black; padding: 2px;">transformer</td> <td style="border: 1px solid black; padding: 2px;">converts a sine wave to a square wave</td> </tr> <tr> <td></td> <td style="border: 1px solid black; padding: 2px;">keeps the DC voltage above a certain value by storing charge on a capacitor to provide electricity to the output when the supply voltage is low</td> </tr> <tr> <td></td> <td style="border: 1px solid black; padding: 2px;">converts electrical energy into mechanical energy</td> </tr> </tbody> </table>	Block	Function	rectifier	produces a constant 5 V regardless of whether it is providing a large current for a flat phone battery or a small current to a fully charged phone	smoothing circuit	reduces the 230 V AC to a much lower AC voltage	stabilising circuit (load regulator)	converts alternating current to direct current	transformer	converts a sine wave to a square wave		keeps the DC voltage above a certain value by storing charge on a capacitor to provide electricity to the output when the supply voltage is low		converts electrical energy into mechanical energy	<p>2</p>	<p>No marks for any block with links to more than one function.</p>
Block	Function																
rectifier	produces a constant 5 V regardless of whether it is providing a large current for a flat phone battery or a small current to a fully charged phone																
smoothing circuit	reduces the 230 V AC to a much lower AC voltage																
stabilising circuit (load regulator)	converts alternating current to direct current																
transformer	converts a sine wave to a square wave																
	keeps the DC voltage above a certain value by storing charge on a capacitor to provide electricity to the output when the supply voltage is low																
	converts electrical energy into mechanical energy																
<p>4 (b)</p>	<p>Correct diode symbol  used anywhere in diagram</p> <p>Diode achieves rectification</p> <p>Rectifier produces correct polarity half-wave rectified dc with one diode</p>	<p>1</p> <p>1</p> <p>1</p>	<p>Accept alternative diode symbol</p> <table border="0" style="width: 100%;"> <tr> <td style="text-align: center;"></td> <td style="text-align: center;"></td> <td style="text-align: center;"></td> </tr> <tr> <td style="text-align: center;"></td> <td style="text-align: center;"></td> <td style="text-align: center;"></td> </tr> </table> <p>Award this mark even if polarity of output is incorrect</p> <p>Must obtain rectification mark for this mark</p> <p>For a correct full-wave rectifier circuit that produces the</p>														
																	
																	

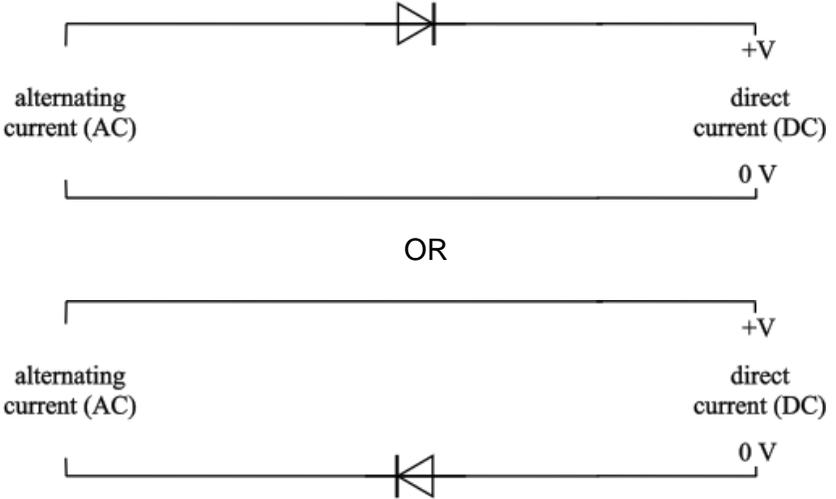Question	Answer	Marks	Guidance
	<p>Correct answers for 3 marks:</p>  <p>OR</p>		<p>required polarity award 2 marks.</p> <p>Accept other correct alternative solutions. Ignore load resistor <u>across</u> output or transformer across input</p>
<p>4 (c)</p>	<p>Direct current: only flows in one direction (owtte)</p> <p>Alternating current: changes direction periodically/moves one way then the other/keeps changing direction (owtte)</p>	<p>1</p> <p>1</p>	<p>Do not accept 'flows in both directions'. Answer must express the idea that the change in direction of current flow changes with time.</p>

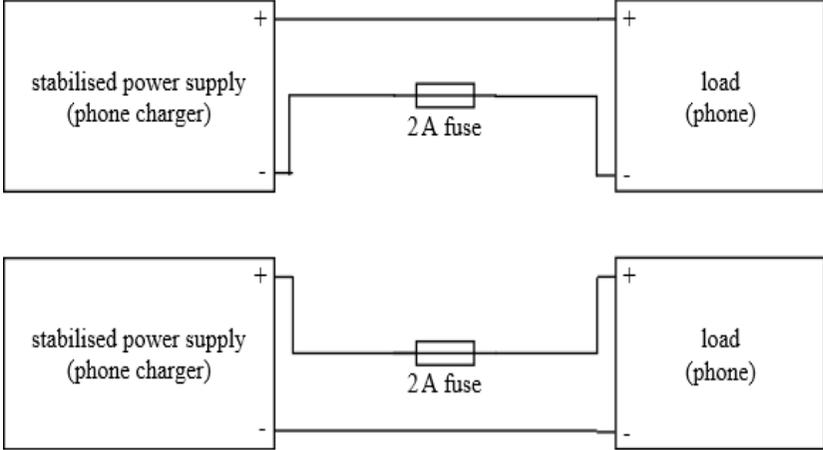Question			Answer	Marks	Guidance
4	(d)	(i)	<p>Either of the below</p>  <p>The top diagram shows a box labeled 'stabilised power supply (phone charger)' with a '+' terminal at the top and a '-' terminal at the bottom. A wire connects the '+' terminal to the '+' terminal of a box labeled 'load (phone)'. A second wire connects the '-' terminal of the power supply to a '2 A fuse' (represented by a rectangle with a diagonal line), which then connects to the '-' terminal of the load. The bottom diagram is similar, but the '2 A fuse' is placed on the wire connecting the '-' terminal of the power supply to the '-' terminal of the load.</p>	1	
4	(d)	(ii)	<p>When too much <u>current</u> flows</p> <p>the thin fuse wire melts</p> <p><u>disconnecting</u> the supply from the load so preventing and damage to the supply or the load.</p>	<p>1</p> <p>1</p> <p>1</p>	<p>Must mention current for this mark. Look for comment about a large current (2 A <u>or more</u>)</p> <p>Look for comment about fuse failing/blowing under adverse conditions</p> <p>Look for comment about disconnecting or preventing further flow of current</p>

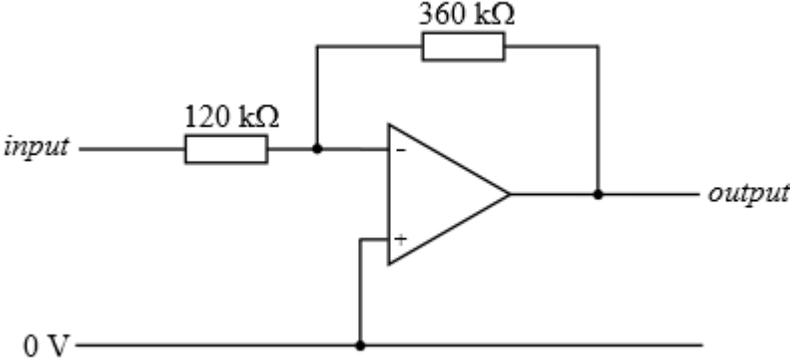Question			Answer	Marks	Guidance
5	(a)	(i)	inverting amplifier	1	
5	(a)	(ii)		1	<p>Must have both correctly labelled for one mark</p> <p>Allow labelling of output anywhere on output line</p> <p>Accept V_{in} and V_{out}</p>
5	(a)	(iii)	$\text{Voltage Gain} = -\frac{R_f}{R_{in}} = -\frac{360000}{120000} = -3$ <p>magnitude sign</p>	<p>1</p> <p>1</p>	<p>Ignore any units</p> <p>1 mark for +3</p> <p>1 mark for a negative number</p>
5	(a)	(iv)	$V_{out} = G \times V_{in} = -3 \times 1.5 = -4.5 \text{ V}$	1	Unit given in question ecf Voltage Gain from 5a(iii)

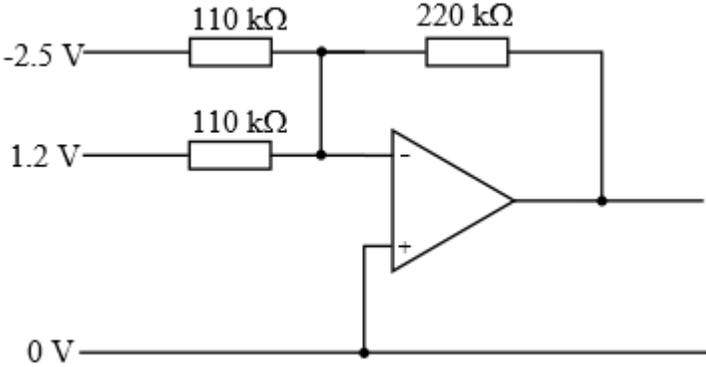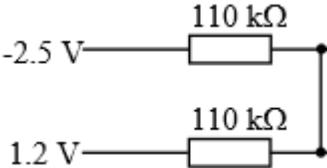Question	Answer	Marks	Guidance
5 (b) (i)	 <p>Op-amp with feedback resistor of 220 kΩ from output to inverting input and non-inverting input to 0 V</p> <p>Two input resistors of 110 kΩ each with inputs labelled -2.5 V and 1.2 V</p>	1 1	<p>Accept any two correctly labelled resistors joined to a common point</p> 
5 (b) (ii)	$V_{\text{out}} = -\frac{R_f}{R_{\text{in}}}(V_1 + V_2) = -\frac{220000}{110000} \times (-2.5 + 1.2) = 2.6 \text{ V}$	1	<p>Correct answer</p> <p>Unit given in question</p>
6 (a)	AND gate	1	

Question		Answer	Marks	Guidance																																				
6	(b)	<table border="1"> <thead> <tr> <th>A</th> <th>D</th> <th>E</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>all combinations of A and D (any order) E correct</p>	A	D	E	0	0	0	0	1	0	1	0	0	1	1	1	2																						
A	D	E																																						
0	0	0																																						
0	1	0																																						
1	0	0																																						
1	1	1																																						
6	(c)	$E = A \cdot D$	1																																					
6	(d)	<table border="1"> <thead> <tr> <th>D</th> <th>E</th> <th>F</th> <th>G</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	D	E	F	G	1	0	0	0	1	0	0	0	0	0	1	1	0	0	0	0	1	1	0	1	1	1	0	1	0	0	1	1	0	0	0	0	1 1 1 1	1 mark for each correct column allow ecf from D to E allow ecf from D to F allow ecf from E and F to G
D	E	F	G																																					
1	0	0	0																																					
1	0	0	0																																					
0	0	1	1																																					
0	0	0	0																																					
1	1	0	1																																					
1	1	0	1																																					
0	0	1	1																																					
0	0	0	0																																					

OCR (Oxford Cambridge and RSA Examinations)
The Triangle Building
Shaftesbury Road
Cambridge
CB2 8EA

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2019

 **Cambridge
Assessment**

