



# Cambridge International AS & A Level

---

**COMPUTER SCIENCE****9608/33**

Paper 3 Written Paper

**May/June 2020**

MARK SCHEME

Maximum Mark: 75

---

**Published**

Students did not sit exam papers in the June 2020 series due to the Covid-19 global pandemic.

This mark scheme is published to support teachers and students and should be read together with the question paper. It shows the requirements of the exam. The answer column of the mark scheme shows the proposed basis on which Examiners would award marks for this exam. Where appropriate, this column also provides the most likely acceptable alternative responses expected from students. Examiners usually review the mark scheme after they have seen student responses and update the mark scheme if appropriate. In the June series, Examiners were unable to consider the acceptability of alternative responses, as there were no student responses to consider.

Mark schemes should usually be read together with the Principal Examiner Report for Teachers. However, because students did not sit exam papers, there is no Principal Examiner Report for Teachers for the June 2020 series.

Cambridge International will not enter into discussions about these mark schemes.

Cambridge International is publishing the mark schemes for the June 2020 series for most Cambridge IGCSE™ and Cambridge International A & AS Level components, and some Cambridge O Level components.

---

This document consists of **8** printed pages.

### Generic Marking Principles

These general marking principles must be applied by all examiners when marking candidate answers. They should be applied alongside the specific content of the mark scheme or generic level descriptors for a question. Each question paper and mark scheme will also comply with these marking principles.

#### GENERIC MARKING PRINCIPLE 1:

Marks must be awarded in line with:

- the specific content of the mark scheme or the generic level descriptors for the question
- the specific skills defined in the mark scheme or in the generic level descriptors for the question
- the standard of response required by a candidate as exemplified by the standardisation scripts.

#### GENERIC MARKING PRINCIPLE 2:

Marks awarded are always **whole marks** (not half marks, or other fractions).

#### GENERIC MARKING PRINCIPLE 3:

Marks must be awarded **positively**:

- marks are awarded for correct/valid answers, as defined in the mark scheme. However, credit is given for valid answers which go beyond the scope of the syllabus and mark scheme, referring to your Team Leader as appropriate
- marks are awarded when candidates clearly demonstrate what they know and can do
- marks are not deducted for errors
- marks are not deducted for omissions
- answers should only be judged on the quality of spelling, punctuation and grammar when these features are specifically assessed by the question as indicated by the mark scheme. The meaning, however, should be unambiguous.

#### GENERIC MARKING PRINCIPLE 4:

Rules must be applied consistently e.g. in situations where candidates have not followed instructions or in the application of generic level descriptors.

#### GENERIC MARKING PRINCIPLE 5:

Marks should be awarded using the full range of marks defined in the mark scheme for the question (however; the use of the full mark range may be limited according to the quality of the candidate responses seen).

#### GENERIC MARKING PRINCIPLE 6:

Marks awarded are based solely on the requirements as defined in the mark scheme. Marks should not be awarded with grade thresholds or grade descriptors in mind.

Question	Answer	Marks
1(a)	= (0)11000000.1 (conversion to binary) [1] = $0.110000001 \times 2^8$ (evidence of shifting binary point appropriately) [1] = 0110000001 001000 (stored as mantissa and exponent) [1]	3
1(b)	1001111110 (one's complement of 10 bit mantissa) [1] 1001111111 (two's complement of 10 bit mantissa) [1] 1001111111 001000 (stored as mantissa and exponent) [1]	3
1(c)	Any <b>three</b> from: <ul style="list-style-type: none"> <li>• Exponent too large to fit in 4 bits as a two's complement number</li> <li>• Exponent will turn negative/−8</li> <li>• ... therefore, point moves the wrong way</li> <li>• Value will be approx. +0.0029(296875)</li> </ul>	3

Question	Answer	Marks
2	<p><b>One mark for each correct line drawn</b></p>	4


Question	Answer	Marks
3(a)(i)	Any <b>three</b> from: <ul style="list-style-type: none"> <li>• A circuit is established at the start of the communication</li> <li>• Between sender and receiver</li> <li>• This lasts for the duration of the call/data transfer</li> <li>• Then the links that make up the circuit are removed</li> </ul>	3
3(a)(ii)	Any <b>two</b> from: <ul style="list-style-type: none"> <li>• A dedicated channel // Not sharing channel</li> <li>• ...can use all bandwidth</li> <li>• Two-way real time conversation</li> <li>• No delay as no switching</li> <li>• Data arrives in order it is sent</li> </ul>	2

Question	Answer	Marks
3(b)(i)	Any <b>three</b> from: <ul style="list-style-type: none"> <li>• A circuit does not have to be established at the start of the communication</li> <li>• The data to be sent is divided into packets</li> <li>• That can travel along different routes</li> <li>• From node to node</li> <li>• Packets are reassembled in the correct order at the receiver's end</li> <li>• Must wait until the last packet is received to put the data back together</li> </ul>	<b>3</b>
3(b)(ii)	Any <b>two</b> from: <ul style="list-style-type: none"> <li>• Communication is asynchronous</li> <li>• Allows for error checking</li> <li>• Real time transmission is not required</li> <li>• Smaller amounts of data are sent (than voice calls) therefore dedicated line/higher bandwidth not required // can share the bandwidth</li> <li>• Doesn't matter if data arrives out of order</li> </ul>	<b>2</b>

Question	Answer	Marks
4(a)	$X = ((P \text{ XOR } Q) \text{ XOR } R)$ $Y = ((P \text{ XOR } Q) \text{ AND } R) \text{ OR } (P \text{ AND } Q)$ or $X = (\overline{P \cdot Q} + P \cdot \overline{Q}) \cdot R + (\overline{P \cdot Q} + P \cdot \overline{Q}) \cdot \overline{R}$ $Y = (\overline{P \cdot Q} + P \cdot \overline{Q}) \cdot R + P \cdot Q$ <b>One</b> mark for correct use of XOR <b>One</b> mark for correct use of AND <b>One</b> mark for correct use of OR <b>One</b> mark for X correct <b>One</b> mark for Y correct	<b>5</b>
4(b)(i)	X: Sum Y: Carry (out)	<b>2</b>
4(b)(ii)	Carry (in)	<b>1</b>

Question	Answer	Marks
5	<ul style="list-style-type: none"> <li>• RISC / reduced instruction set computer</li> <li>• CISC / complex instruction set computer</li> <li>• Pipelining</li> </ul>	<b>3</b>

Question	Answer	Marks
6(a)	$P \cdot Q + P \cdot \overline{Q} - *$ <b>One</b> mark for $P \cdot Q +$ <b>One</b> mark for $P \cdot \overline{Q} - *$	<b>2</b>

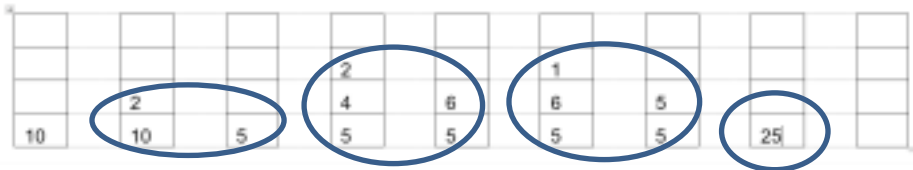Question	Answer	Marks
6(b)(i)	 <p>One mark for each correct stack after a calculation</p>	4
6(b)(ii)	$((P + Q) * M) - (R - P)$ One mark for $((P + Q) * M)$ One mark for $-(R - P)$	2
6(c)	Any <b>two</b> from: <ul style="list-style-type: none"> <li>Expressions are always evaluated left to right</li> <li>Each operator uses the two previous values on the stack (except unary minus)</li> <li>Description of pushing and popping on a stack</li> </ul>	2

Question	Answer	Marks
7(a)	For each task: One mark for correct state One mark for suitable reason <ul style="list-style-type: none"> <li>Temperature: ready</li> <li>Reason: waiting for the 10 seconds to be finished</li> <li>Windspeed: running</li> <li>Reason: it is currently recording the windspeed</li> <li>Sending: blocked</li> <li>Reason: it is waiting for the internet connection</li> </ul>	6
7(b)	Any <b>four</b> from: <ul style="list-style-type: none"> <li>Uses a timer // uses two timers</li> <li>Each timer is continually checked to see if 10 seconds has passed</li> <li>...if it has, an interrupt is sent to the OS</li> <li>...OS checks interrupt status</li> <li>...and may pass control to the interrupt handling routine</li> <li>(If 10 seconds has passed) then the ISR switches process state to running/ready</li> <li>When finished it passes control back to OS</li> <li>The timer is restarted</li> </ul>	4

Question	Answer	Marks
8(a)	Any <b>three</b> from: <ul style="list-style-type: none"> <li>a hashing algorithm</li> <li>a public key</li> <li>serial number</li> <li>dates valid</li> </ul>	3

Question	Answer	Marks																																																																																
8(b)	<p>Any <b>six</b> from:</p> <ul style="list-style-type: none"> <li>• Martha's message is encrypted using Joshua's public key (provided by Joshua's digital certificate).</li> <li>• Martha's hashing algorithm is used on the message to produce the message digest.</li> <li>• The message digest is then encrypted with Martha's private key to provide a digital signature.</li> <li>• Both the encrypted message and the digital signature are sent.</li> <li>• The message is decrypted with Joshua's private key.</li> <li>• Martha's digital signature is decrypted with Martha's public key (provided by the Martha's digital certificate) to obtain the message digest.</li> <li>• Martha's hashing algorithm (provided by the Martha's digital certificate) recreates the message digest from the decrypted message.</li> <li>• The two message digests are compared, if they are the same then the message should be authentic/has not been tampered.</li> </ul>	<b>6</b>																																																																																
9(a)	<table border="1" data-bbox="347 853 1209 1227"> <tbody> <tr> <td>501</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>Door 1</td> </tr> <tr> <td>502</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>Door 2</td> </tr> <tr> <td>503</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>Door 3</td> </tr> <tr> <td>504</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>Door 4</td> </tr> <tr> <td>505</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>Door 5</td> </tr> <tr> <td>506</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>Door 6</td> </tr> <tr> <td>507</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>Door 7</td> </tr> <tr> <td>508</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>Door 8</td> </tr> </tbody> </table> <p><b>One</b> mark for open doors correct <b>One</b> mark for closed doors correct</p>	501	1	1	1	1	1	1	1	1	Door 1	502	0	0	0	0	0	0	0	0	Door 2	503	0	0	0	0	0	0	0	0	Door 3	504	1	1	1	1	1	1	1	1	Door 4	505	0	0	0	0	0	0	0	0	Door 5	506	0	0	0	0	0	0	0	0	Door 6	507	1	1	1	1	1	1	1	1	Door 7	508	0	0	0	0	0	0	0	0	Door 8	<b>2</b>
501	1	1	1	1	1	1	1	1	Door 1																																																																									
502	0	0	0	0	0	0	0	0	Door 2																																																																									
503	0	0	0	0	0	0	0	0	Door 3																																																																									
504	1	1	1	1	1	1	1	1	Door 4																																																																									
505	0	0	0	0	0	0	0	0	Door 5																																																																									
506	0	0	0	0	0	0	0	0	Door 6																																																																									
507	1	1	1	1	1	1	1	1	Door 7																																																																									
508	0	0	0	0	0	0	0	0	Door 8																																																																									

Question	Answer	Marks																																																																	
9(b)(i)	<table border="1" data-bbox="466 286 1163 1088"> <thead> <tr> <th colspan="3" data-bbox="466 286 924 347">Instruction</th> <th data-bbox="924 286 1038 347">ACC</th> <th data-bbox="1038 286 1163 347">501</th> </tr> <tr> <th data-bbox="466 347 632 407">Label</th> <th data-bbox="632 347 772 407">Op code</th> <th data-bbox="772 347 924 407">Operand</th> <th data-bbox="924 347 1038 407"></th> <th data-bbox="1038 347 1163 407"></th> </tr> </thead> <tbody> <tr> <td data-bbox="466 407 632 470">CHECK1 :</td> <td data-bbox="632 407 772 470">LDD</td> <td data-bbox="772 407 924 470">500</td> <td data-bbox="924 407 1038 470">&amp;AA</td> <td data-bbox="1038 407 1163 470"></td> </tr> <tr> <td data-bbox="466 470 632 533"></td> <td data-bbox="632 470 772 533">AND</td> <td data-bbox="772 470 924 533">&amp;80</td> <td data-bbox="924 470 1038 533">&amp;80</td> <td data-bbox="1038 470 1163 533"></td> </tr> <tr> <td data-bbox="466 533 632 595"></td> <td data-bbox="632 533 772 595">CMP</td> <td data-bbox="772 533 924 595">&amp;00</td> <td data-bbox="924 533 1038 595"></td> <td data-bbox="1038 533 1163 595"></td> </tr> <tr> <td data-bbox="466 595 632 658"></td> <td data-bbox="632 595 772 658">JPE</td> <td data-bbox="772 595 924 658">DOOR1</td> <td data-bbox="924 595 1038 658"></td> <td data-bbox="1038 595 1163 658"></td> </tr> <tr> <td data-bbox="466 658 632 721"></td> <td data-bbox="632 658 772 721">LDM</td> <td data-bbox="772 658 924 721">&amp;FF</td> <td data-bbox="924 658 1038 721">&amp;FF</td> <td data-bbox="1038 658 1163 721"></td> </tr> <tr> <td data-bbox="466 721 632 784">DOOR1 :</td> <td data-bbox="632 721 772 784">STO</td> <td data-bbox="772 721 924 784">501</td> <td data-bbox="924 721 1038 784"></td> <td data-bbox="1038 721 1163 784">&amp;FF</td> </tr> <tr> <td data-bbox="466 784 632 846"></td> <td data-bbox="632 784 772 846">WAIT</td> <td data-bbox="772 784 924 846"></td> <td data-bbox="924 784 1038 846"></td> <td data-bbox="1038 784 1163 846"></td> </tr> <tr> <td data-bbox="466 846 632 909"></td> <td data-bbox="632 846 772 909">LDM</td> <td data-bbox="772 846 924 909">&amp;00</td> <td data-bbox="924 846 1038 909">&amp;00</td> <td data-bbox="1038 846 1163 909"></td> </tr> <tr> <td data-bbox="466 909 632 972"></td> <td data-bbox="632 909 772 972">STO</td> <td data-bbox="772 909 924 972">501</td> <td data-bbox="924 909 1038 972"></td> <td data-bbox="1038 909 1163 972">&amp;00</td> </tr> <tr> <td data-bbox="466 972 632 1034"></td> <td data-bbox="632 972 772 1034">WAIT</td> <td data-bbox="772 972 924 1034"></td> <td data-bbox="924 972 1038 1034"></td> <td data-bbox="1038 972 1163 1034"></td> </tr> <tr> <td data-bbox="466 1034 632 1088"></td> <td data-bbox="632 1034 772 1088">JMP</td> <td data-bbox="772 1034 924 1088">CHECK1</td> <td data-bbox="924 1034 1038 1088"></td> <td data-bbox="1038 1034 1163 1088"></td> </tr> </tbody> </table> <p data-bbox="316 1153 842 1220"><b>Two</b> marks for all values of ACC correct Or <b>One</b> mark for 3 values of ACC correct</p> <p data-bbox="316 1288 871 1355"><b>Two</b> marks for both values of 501 correct Or <b>One</b> mark for one value of 501 correct</p>	Instruction			ACC	501	Label	Op code	Operand			CHECK1 :	LDD	500	&AA			AND	&80	&80			CMP	&00				JPE	DOOR1				LDM	&FF	&FF		DOOR1 :	STO	501		&FF		WAIT					LDM	&00	&00			STO	501		&00		WAIT					JMP	CHECK1			<b>4</b>
Instruction			ACC	501																																																															
Label	Op code	Operand																																																																	
CHECK1 :	LDD	500	&AA																																																																
	AND	&80	&80																																																																
	CMP	&00																																																																	
	JPE	DOOR1																																																																	
	LDM	&FF	&FF																																																																
DOOR1 :	STO	501		&FF																																																															
	WAIT																																																																		
	LDM	&00	&00																																																																
	STO	501		&00																																																															
	WAIT																																																																		
	JMP	CHECK1																																																																	

Question	Answer	Marks																																							
9(b)(ii)	<table border="1" data-bbox="466 250 1163 1052"> <thead> <tr> <th colspan="3" data-bbox="466 250 1163 311">Instruction</th> </tr> <tr> <th data-bbox="466 311 746 371">Label</th> <th data-bbox="746 311 916 371">Op code</th> <th data-bbox="916 311 1163 371">Operand</th> </tr> </thead> <tbody> <tr> <td data-bbox="466 371 746 432">CHECK2 :</td> <td data-bbox="746 371 916 432">LDD</td> <td data-bbox="916 371 1163 432">500</td> </tr> <tr> <td data-bbox="466 432 746 492"></td> <td data-bbox="746 432 916 492">AND</td> <td data-bbox="916 432 1163 492">&amp;40</td> </tr> <tr> <td data-bbox="466 492 746 553"></td> <td data-bbox="746 492 916 553">CMP</td> <td data-bbox="916 492 1163 553">&amp;00</td> </tr> <tr> <td data-bbox="466 553 746 613"></td> <td data-bbox="746 553 916 613">JPE</td> <td data-bbox="916 553 1163 613">DOOR2</td> </tr> <tr> <td data-bbox="466 613 746 674"></td> <td data-bbox="746 613 916 674">LDM</td> <td data-bbox="916 613 1163 674">&amp;FF</td> </tr> <tr> <td data-bbox="466 674 746 734">DOOR2 :</td> <td data-bbox="746 674 916 734">STO</td> <td data-bbox="916 674 1163 734">502</td> </tr> <tr> <td data-bbox="466 734 746 795"></td> <td data-bbox="746 734 916 795">WAIT</td> <td data-bbox="916 734 1163 795"></td> </tr> <tr> <td data-bbox="466 795 746 855"></td> <td data-bbox="746 795 916 855">LDM</td> <td data-bbox="916 795 1163 855">&amp;00</td> </tr> <tr> <td data-bbox="466 855 746 916"></td> <td data-bbox="746 855 916 916">STO</td> <td data-bbox="916 855 1163 916">502</td> </tr> <tr> <td data-bbox="466 916 746 976"></td> <td data-bbox="746 916 916 976">WAIT</td> <td data-bbox="916 916 1163 976"></td> </tr> <tr> <td data-bbox="466 976 746 1037"></td> <td data-bbox="746 976 916 1037">JMP</td> <td data-bbox="916 976 1163 1037">CHECK2</td> </tr> </tbody> </table> <p data-bbox="316 1086 821 1220"> <b>One</b> mark for correct LDM values  <b>One</b> mark for correct AND value  <b>One</b> mark for correct labels and jumps  <b>One</b> mark for fully correct code         </p>	Instruction			Label	Op code	Operand	CHECK2 :	LDD	500		AND	&40		CMP	&00		JPE	DOOR2		LDM	&FF	DOOR2 :	STO	502		WAIT			LDM	&00		STO	502		WAIT			JMP	CHECK2	4
Instruction																																									
Label	Op code	Operand																																							
CHECK2 :	LDD	500																																							
	AND	&40																																							
	CMP	&00																																							
	JPE	DOOR2																																							
	LDM	&FF																																							
DOOR2 :	STO	502																																							
	WAIT																																								
	LDM	&00																																							
	STO	502																																							
	WAIT																																								
	JMP	CHECK2																																							
9(c)	<ul data-bbox="316 1254 1257 1321" style="list-style-type: none"> <li>• Either the value in 500 is always zero which means the light is off</li> <li>• Or it alternates between zero (light off) and 1 (light on) every second</li> </ul>	2																																							